


# Concepts of Experiments at Future Colliders II

PD Dr. Oliver Kortner

26.04.2024

# Recapitulation of the previous lecture
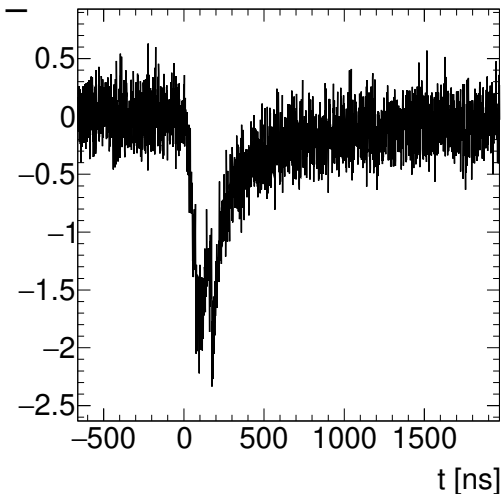
## Introductory example: cylindrical drift tube



- Particle detectors provide **current or voltage pulses**, which contain information about particle passage or deposited energy.
- To obtain this information, they must be processed electronically.

## Analog and digital signals

**Analog signal:** Information contained in the continuous variation of electrical signal properties, e.g., pulse height, pulse duration, or pulse shape.

**Digital signal:** Information stored in discrete form.

Example. TTL (Transistor-Transistor Logic):


Logical 0: Signal between 0 and 0.8 V.

Logical 1: Signal between 2 V and 5 V.

Advantage of a digital signal: No information loss with small signal disturbances.

# Recapitulation of the previous lecture

## Characteristics of a signal pulse

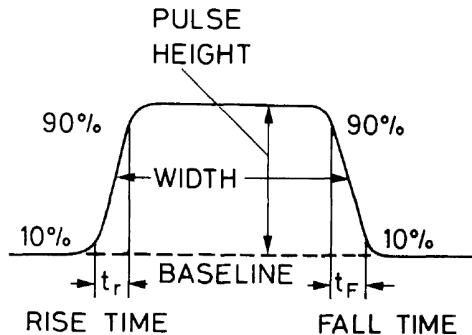


Slow Signal:  $t_A \gtrsim 100$  ns.

Fast Signal:  $t_A \lesssim 1$  ns.

# Recapitulation of the previous lecture

Deformed rectangular pulse

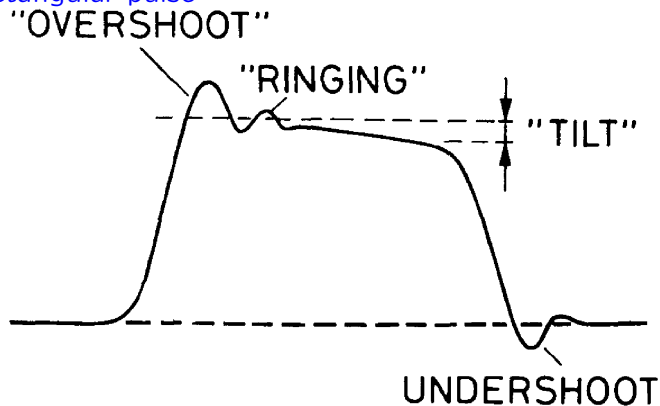

# Recapitulation of the previous lecture

## Attenuation and bandwidth


### Attenuation



$$\text{Attenuation [dB]} := 10 \cdot \log_{10} \left( \frac{|\hat{s}_A|^2}{|\hat{s}_E|^2} \right).$$

$$-3 \text{ dB} = 10 \cdot \log_{10} \left( \frac{|\hat{s}_A|^2}{|\hat{s}_E|^2} \right) \Leftrightarrow \frac{|\hat{s}_A|^2}{|\hat{s}_E|^2} = 10^{-\frac{3}{10}} = \frac{1}{2}.$$

### Bandwidth

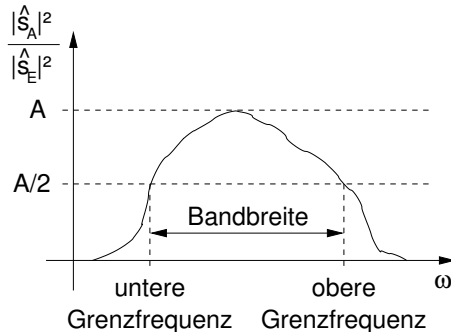

## Passive electronic components – Ohmic resistance

### Drude's model of electrical conduction in metals

Metals are electrical conductors. In an ideal conductor, the conduction electrons experience no resistance. In a real conductor, they collide with the atomic nuclei.

#### Assumptions

- Neglect of interaction between the conduction electrons.
- Free electron motion between collisions with atomic nuclei.
  - Non-accelerated motion in between collisions.
- Elastic collisions between conduction electrons and atomic nuclei.  
The conduction electrons are not heated by the collisions.

# Recapitulation of the previous lecture

## Electron movement in the Drude model

Equation of motion of a conduction electron:

$$m_e \cdot \frac{d\vec{v}}{dt} = -e\vec{E}.$$


$\tau$ : Average time between two collisions off atoms.

$$\langle \vec{v} \rangle = -\frac{e}{m_e} \vec{E} \cdot \tau + \underbrace{\langle \vec{v}_0 \rangle}_{=0 \text{ (in therm. equ.)}} = -\frac{e}{m_e} \tau \cdot \vec{E}.$$

$n$ : Conduction electron density.

$L$ : Length of the real conductor.

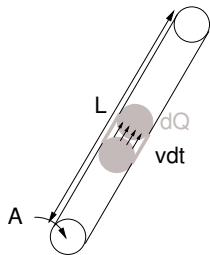$A$ : Cross section of the real conductor.



$$dQ = -n \cdot e |\vec{v}| \cdot dt \cdot A \Leftrightarrow I = \frac{dQ}{dt} = -nev \cdot A = \frac{ne^2\tau}{m_e} \cdot A \cdot E.$$

Hence

$$\vec{j} = \frac{ne^2\tau}{m_e} \cdot \vec{E} =: \sigma \cdot \vec{E}.$$

$\sigma$ : electric conductivity.



# Recapitulation of the previous lecture

## Ohm's law

Voltage between the ends of the conductor:



$$U = L \cdot \underbrace{E}_{= \frac{I}{\sigma \cdot A}} = \frac{L}{\sigma \cdot A} \cdot I =: R \cdot I \text{ (Ohm's Law)}.$$

## Ohmic resistance

$$R = \frac{L}{\sigma \cdot A} =: \rho \cdot \frac{L}{A}.$$

$\rho$ : specific resistance (unit:  $\Omega\text{cm}$ ).

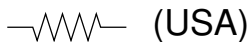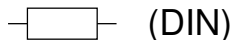Schematic symbols for an ohmic resistance:



# Recapitulation of the previous lecture

## Passive electronic components – capacitance

$$C = \frac{Q}{U} \Rightarrow \text{No current flow at DC voltage.}$$

Current flow at AC voltage:

$$\frac{dU}{dt} = \frac{dQ}{dt} = \frac{I}{C}.$$

Transition to frequency representation:

$$U(t) = \frac{1}{\sqrt{2\pi}} \int_{-\infty}^{\infty} \hat{U}(\omega) e^{i\omega t} d\omega, \quad I(t) = \frac{1}{\sqrt{2\pi}} \int_{-\infty}^{\infty} \hat{I}(\omega) e^{i\omega t} d\omega.$$

$$\frac{dU}{dt} = \frac{1}{\sqrt{2\pi}} \int_{-\infty}^{\infty} i\omega \hat{U}(\omega) e^{i\omega t} d\omega = \frac{I(t)}{C} = \frac{1}{\sqrt{2\pi}} \int_{-\infty}^{\infty} \frac{1}{C} \hat{I}(\omega) e^{i\omega t} d\omega,$$

leading to  $i\omega \hat{U}(\omega) = \frac{1}{C} \hat{I}(\omega)$ , thus  $\hat{U}(\omega) = \frac{1}{i\omega C} \hat{I}(\omega)$ .

Capacitance – impedance and schematic symbol

$$\hat{U}(\omega) = \frac{1}{i\omega C} \hat{I}(\omega).$$

Impedance:  $Z_C = \frac{1}{i\omega C}$ .


Schematic symbol:



## Reminder: Field inside an ideal coil

$\frac{dN}{dl}$ : Number of turns per unit length.

Ampère's law:

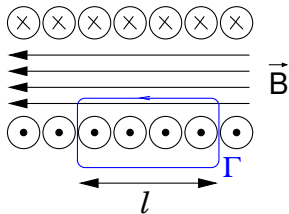

$$\oint_{\Gamma} \vec{B} \cdot d\vec{s} = l \cdot B = \mu_0 \cdot I \cdot \frac{dN}{dl} \cdot l.$$


$$B = \mu_0 \frac{dN}{dl} \cdot I =: \frac{1}{A} L \cdot I.$$

$A$ : Cross-sectional area of the coil.

$L$ : Inductance.

# Recapitulation of the previous lecture

## Ideal toroidal coil

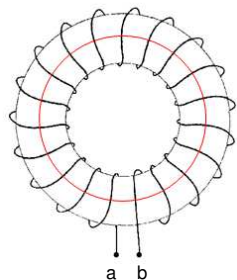

- $B$  exists only inside the coil.
- If the coil is made of an ideal conductor,  $\vec{E}$  inside the conductor is 0. Otherwise, an infinitely large current would flow through the conductor.

$$\Rightarrow U_{ab} = 0.$$

- With alternating current, because  $\frac{dI}{dt} \neq 0$ ,  $\frac{\partial B}{\partial t} \neq 0$ , resulting in a non-zero electromotive force.

$$\text{curl } \vec{E} = -\frac{\partial \vec{B}}{\partial t}.$$

$$U_{ab} = \oint \vec{E} \cdot d\vec{s} = \int_A \text{curl } \vec{E} d\vec{A} = - \int_A \frac{\partial \vec{B}}{\partial t} \cdot d\vec{A} = -\frac{\partial}{\partial t} B \cdot A = -\frac{\partial}{\partial t} \frac{1}{A} LIA = -L \frac{dI}{dt}.$$

In the frequency domain, we have  $\hat{U}(\omega) = -i\omega L \hat{I}(\omega)$ .

## Inductance – impedance and circuit symbol

$$\hat{U}(\omega) = -i\omega L\hat{I}(\omega).$$

Impedance:  $Z_L = -i\omega L$ .


Circuit Symbol:  (DIN)

 (USA)

**Remark.** In the frequency domain, the behavior of a circuit containing the mentioned passive elements can be calculated in a similar manner to a circuit containing ohmic resistances, by using impedances.
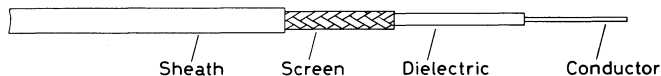
## Signal transmission

Explanatory example: signal transmission via a coaxial cable




Due to their shielding, coaxial cables do not emit electromagnetic waves. However, they can intercept electromagnetic interference from the surroundings through their shielding.

# Recapitulation of the previous lecture
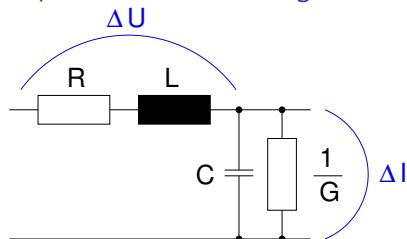
## Signal propagation in a coaxial cable

Equivalent circuit diagram for a  $\Delta z$  length segment of a coaxial cable



$R$ ,  $L$ ,  $C$ ,  $\frac{1}{G}$  represent resistance, inductance, capacitance, and conductance per unit length, respectively.

In an ideal cable,  $R$  and  $G$  are both equal to 0.

## Derivation of the general wave equation for a coaxial cable

$$\Delta U = -(R \cdot \Delta z) \cdot I - (L \cdot \Delta z) \cdot \frac{\partial I}{\partial t}.$$

$$\Delta I = -\left(\frac{1}{G} \cdot \Delta z\right) \cdot U - (C \cdot \Delta z) \cdot \frac{\partial U}{\partial t}.$$

Dividing by  $\Delta z$  and taking the limit as  $\Delta z \rightarrow 0$  yields

$$\frac{\partial U}{\partial z} = -R \cdot I - L \cdot \frac{\partial I}{\partial t},$$
$$\frac{\partial I}{\partial z} = -\frac{1}{G} \cdot U - C \cdot \frac{\partial U}{\partial t}.$$



# Recapitulation of the previous lecture

## Wave equation for a coaxial cable

$$\begin{aligned}\frac{\partial U}{\partial z} &= -R \cdot I - L \cdot \frac{\partial I}{\partial t}, & \left| \frac{\partial}{\partial z} \right. \\ \frac{\partial I}{\partial z} &= -\frac{1}{G} \cdot U - C \cdot \frac{\partial U}{\partial t}. & \left| \frac{\partial}{\partial t} \right.\end{aligned}$$

---

$$\begin{aligned}\frac{\partial^2 U}{\partial z^2} &= -R \cdot \frac{\partial I}{\partial z} - L \frac{\partial^2 I}{\partial z \partial t}, \\ \frac{\partial^2 I}{\partial z \partial t} &= -\frac{1}{G} \cdot \frac{\partial U}{\partial t} - C \cdot \frac{\partial^2 U}{\partial t^2}.\end{aligned}$$

---

$$\frac{\partial^2 U}{\partial z^2} = LC \frac{\partial^2 U}{\partial t^2} + (LG + RC) \frac{\partial U}{\partial t} + RGU.$$

Ideal cable:  $R=0, G=0.$

$$\frac{\partial^2 U}{\partial z^2} = LC \frac{\partial^2 U}{\partial t^2}$$

(Wave equation with  $v = \frac{1}{\sqrt{LC}}$ ).

## Properties of a coaxial cable


- In a real cable,  $G$  is very close to 0.
- In a real cable,  $R \neq 0$  leads to dispersion. In practice, the cables used are usually so short that dispersion can be neglected, so  $R = 0$  can be assumed.
- $L = \frac{\mu}{2\pi} \ln \frac{b}{a}$  [H/m],  $C = \frac{2\pi\epsilon}{\ln \frac{b}{a}}$  [F/m].

$$\Rightarrow v = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\mu\epsilon}}.$$

Thus, the choice of dielectric determines  $v$ .

- Characteristic impedance:  $Z := \frac{dU}{dI} = \sqrt{\frac{L}{C}}$ .  
The characteristic impedance depends on the geometry of the cable, i.e., its inner and outer diameter as well as the dielectric used.

# Reflections at the ends of the cables

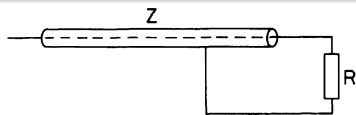

$$U(t, x) = f(x - vt) + g(x + vt),$$

representing an incoming + reflected wave.

Input signal:  $U_E, I_E, Z = \frac{U_E}{I_E}$ .

Reflected signal:  $U_R, I_R, Z = \frac{U_R}{I_R}$ .

Voltage drop across the resistor  $R$ :  $U_E + U_R$ .

Current through  $R$ :  $I_E + I_R$ .

$$\Rightarrow R = \frac{U_E + U_R}{I_E - I_R} = \frac{U_E \left(1 + \frac{U_R}{U_E}\right)}{I_E \left(1 - \frac{I_R}{I_E}\right)} = Z \frac{1 + \rho}{1 - \rho}$$

with the reflection coefficient  $\rho := \frac{U_R}{U_E} = \frac{I_R}{I_E}$ . It holds  $\rho = \frac{R-Z}{R+Z}$ .

- Open cable:  $R = \infty$ .  $\rho = 1$ . Complete reflection at the cable end.
- Short-circuited cable:  $R = 0$ .  $\rho = -1$ . Reflection with opposite amplitude.
- Terminated cable:  $R = Z$ .  $\rho = 0$ . No reflection.

- The analog signals from particle detectors are usually very small.

Example: MDT drift tube filled with Ar/CO<sub>2</sub> (93:7) at 3 bar.

$$\frac{dE}{dx} = 7.5 \text{ keV/cm} \approx 7.5/0.03 = 250 \text{ Electron ion pair/cm.}$$


At a gas gain of 20,000 this corresponds a total charge of only  $\sim 1$  pC.

- ⇒ Protection of small signals by a Faraday cage.
- ⇒ Amplification of signals.
- ⇒ Transmission of unamplified signal over as short as possible distances.

# A Faraday cage in electrostatics

- No electric field inside a conductors, otherwise there would be a current.
- The electric field in a region perfectly enclosed by a conducting cavity equals 0.

Proof by contradiction.

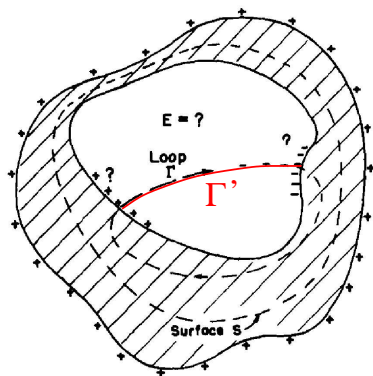

If  $E$  were non-zero inside the cavity, there would be a path  $\Gamma'$  for which  $\int_{\Gamma'} \vec{E} \cdot d\vec{s} \neq 0$ .

Since  $\vec{E} = 0$  inside the conductor, then  $\oint_{\Gamma} \vec{E} \cdot d\vec{s} = \int_{\Gamma'} \vec{E} \cdot d\vec{s} \neq 0$ , which contradicts  $\text{rot } \vec{E} = 0$ .

(Fig.5-12 from Feynman lectures Vol 2)

## 1. Equation of motion underlying the Drude model

$$m_e \frac{d\vec{v}}{dt} = -\frac{m_e}{\tau} \vec{v} - e\vec{E}.$$

Considering  $\vec{E}(t, \vec{x}) = \vec{E}(\omega, \vec{x})e^{-i\omega t}$ , then  $\vec{v}(t, \vec{x}) = \vec{v}(\vec{x})e^{-i\omega t}$ , and we obtain

$$\vec{v}(\vec{x}) = \frac{-e\tau}{m_e} \frac{1}{1 - i\omega\tau} \vec{E}(\omega, \vec{x}),$$

leading to

$$\vec{j} = -ne\vec{v} = \frac{e^2\tau}{m_e} \frac{1}{1 - i\omega\tau} \vec{E} =: \underbrace{\frac{\sigma_0}{1 - i\omega\tau}}_{=: \sigma(\omega)} \vec{E}$$

# Functioning of a Faraday cage in alternating fields

## 2. Maxwell's equations for electromagnetic fields in conductors

$$\operatorname{div} \vec{E} = 0. \quad \operatorname{div} \vec{B} = 0. \quad \operatorname{rot} \vec{E} = -\frac{\partial \vec{B}}{\partial t}. \quad \operatorname{rot} \vec{B} = \frac{1}{c^2 \epsilon_0} \vec{j} + \frac{1}{c^2} \frac{\partial \vec{E}}{\partial t}.$$

$$\operatorname{rot}(\operatorname{rot} \vec{E}) = \operatorname{grad}(\underbrace{\operatorname{div} \vec{E}}_{=0}) - \Delta \vec{E} = \operatorname{rot} \left( -\frac{\partial \vec{B}}{\partial t} \right) = -\frac{\partial}{\partial t} \operatorname{rot} \vec{B}.$$

Now, utilizing  $\vec{j} = \sigma(\omega) \vec{E}$  for  $\vec{E}(t, \vec{x}) = \vec{E}(\omega, \vec{k}) e^{-i(\omega t - \vec{k} \cdot \vec{x})}$ , we obtain

$$|\vec{k}|^2 = \frac{\omega^2}{c^2} \left[ 1 + i \frac{\sigma(\omega)}{\epsilon_0 \omega} \right].$$

$\sigma(\omega) = \frac{\sigma_0}{1 - i\omega\tau} \xrightarrow{\omega\tau \gg 1} \frac{i\sigma_0}{\omega\tau}$ , thus

$$|\vec{k}|^2 = \frac{\omega^2}{c^2} \left( 1 - \frac{\sigma_0}{\epsilon_0 \omega^2 \tau} \right) = \frac{\omega^2}{c^2} \left( 1 - \frac{ne^2}{\epsilon_0 \omega^2} \right),$$

which is negative for  $\omega < \frac{ne^2}{\epsilon_0}$ . Then,  $|\vec{k}|$  is imaginary and the electric field exponentially decreases with increasing penetration into the conductor.


## Conclusions

- Even alternating fields can be shielded by a Faraday cage if their frequency does not become too high.
- For example, choosing aluminum or brass as sufficiently thick material for the Faraday cage, one can shield fields up to the gigahertz range.



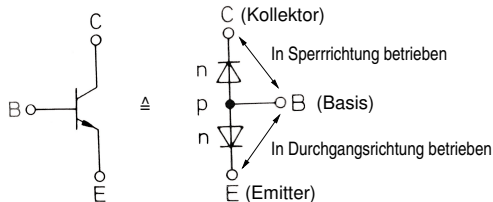
# Bipolar transistor as an example of a signal amplifier

A bipolar transistor is an npn or pnp junction with 3 terminals.




Polarity of an npn transistor

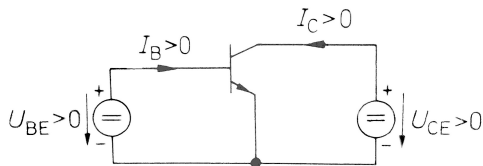

Increasing  $U_{BE}$  reduces the voltage between the base and collector, causing diode BC to conduct more and thus allowing more current to flow from the emitter than has flowed into the base.

- A bipolar transistor is a current amplifier with the current amplification  $B = \frac{I_C}{I_B}$ .
- The value of  $B$  depends on the values of the applied voltages.
- In practice, one is interested in the amplification of small signals. To achieve this, these small signals are superimposed on a DC voltage that sets the operating point of the transistor.
- Since  $B$  fluctuates from one transistor to another, the amplification is determined by the circuitry of the transistor, as explained in the following examples.
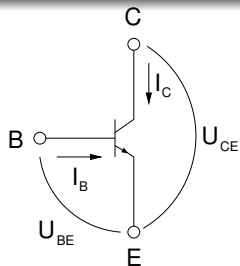
# Basic equations for small-signal amplification



**Goal:** Amplification of small, time-varying signals.

$$dI_B = \left. \frac{\partial I_B}{\partial U_{BE}} \right|_{U_{CE}} \cdot dU_{BE} + \left. \frac{\partial I_B}{\partial U_{CE}} \right|_{U_{BE}} \cdot dU_{CE},$$


$$dI_C = \left. \frac{\partial I_C}{\partial U_{BE}} \right|_{U_{CE}} \cdot dU_{BE} + \left. \frac{\partial I_C}{\partial U_{CE}} \right|_{U_{BE}} \cdot dU_{CE}.$$

- $\frac{1}{r_{BE}} := \left. \frac{\partial I_B}{\partial U_{BE}} \right|_{U_{CE}}$  is small.  $\left. \frac{\partial I_B}{\partial U_{CE}} \right|_{U_{BE}} \approx 0$ .
- Slope  $S := \left. \frac{\partial I_C}{\partial U_{BE}} \right|_{U_{CE}}$  is large.  $\frac{1}{r_{CE}} := \left. \frac{\partial I_C}{\partial U_{CE}} \right|_{U_{BE}}$  is small.

$$\Rightarrow dI_B = \frac{1}{r_{BE}} \cdot dU_{BE},$$


$$dI_C = S \cdot dU_{BE} + \frac{1}{r_{CE}} \cdot dU_{CE}.$$
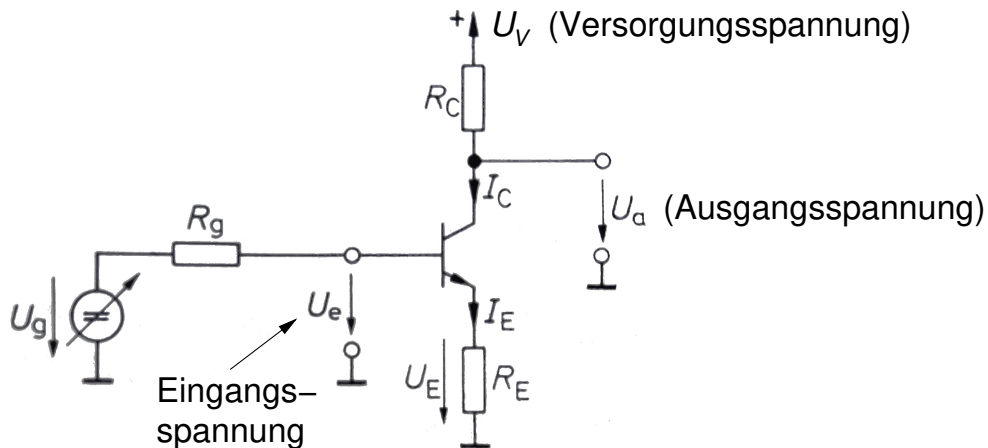
# 1st Example: Emitter circuit with current feedback


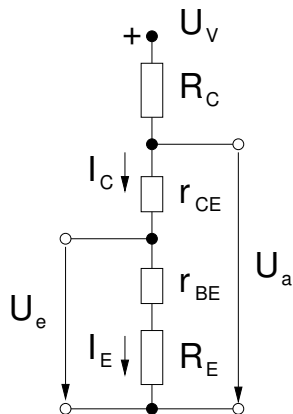
# Calculation of small-signal amplification

Equivalent circuit for calculating the small-signal amplification  $A := \frac{dU_a}{dU_e}$




$$dI_E = \frac{dU_e}{r_{BE} + R_E} \underset{r_{BE} \ll R_E}{\approx} \frac{dU_e}{R_E}.$$

$$dI_C = \frac{d(U_V - U_a)}{R_C} \underset{dU_V=0}{=} -\frac{dU_a}{R_C}.$$

$$dI_E = dI_C \Rightarrow A = \frac{dU_a}{dU_e} = -\frac{R_C}{R_E}.$$


The circuit is inverting with a small-signal amplification that depends only on the configuration of the transistor, namely  $R_C$  and  $R_E$ .
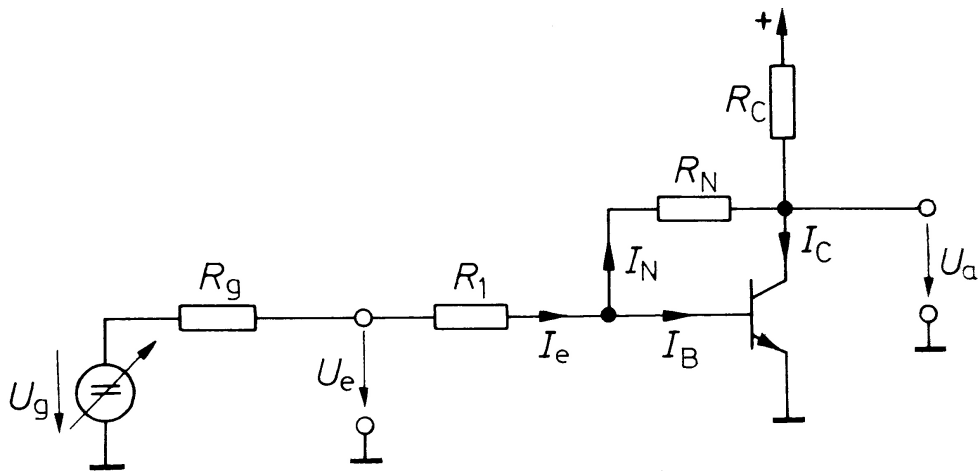
## 2nd Example: Emitter circuit with voltage feedback


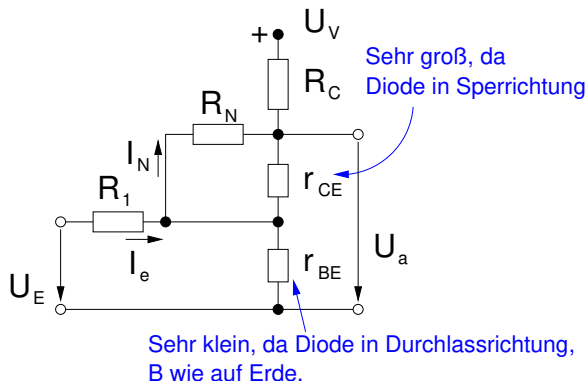
# Calculation of small-signal amplification

Equivalent circuit for calculating the small-signal amplification  $A := \frac{dU_a}{dU_e}$




$$dU_e = R_1 dI_e, \quad dU_a = R_N dI_N = -R_N dI_E.$$
$$\Rightarrow A = \frac{dU_a}{dU_e} = \frac{-R_N}{R_1}.$$

The circuit is inverting with a small-signal amplification that depends only on the configuration of the transistor, namely  $R_N$  and  $R_1$ .
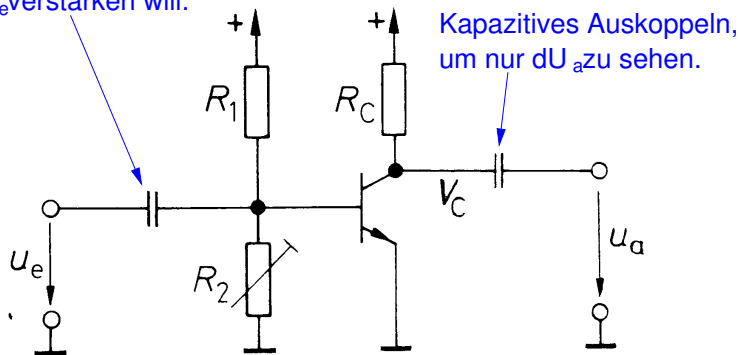
# Operating point adjustment


Kapazitives Einkoppeln des Signals, um den Arbeitspunkt nicht zu verschieben. Möglich, da man nur  $dU_e$  verstärken will.



Spannungsteiler zur Festlegung des Arbeitspunktes des Transistors



# Operation of a differential amplifier

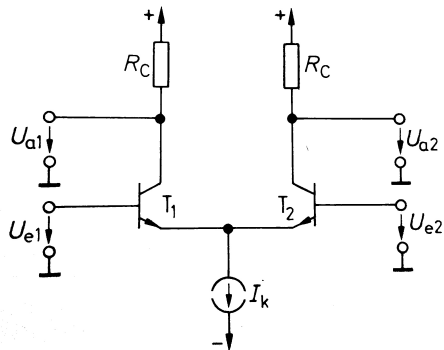

- Constant current source at the emitter.  $\Rightarrow dI_k = 0$ .
- Internal resistance of the constant current source:  $r_k$ .


- $I_k = I_{C1} + I_{C2} \Rightarrow dI_{C1} = -dI_{C2}$ .
- So  $dU_{a1} = -dU_{a2}$ .
- Also  
 $dU_{e1} = dU_{BE1} = -dU_{BE2} = -dU_{e2}$ .
- $U_D := U_{e1} - U_{e2}$ .  
 $dU_{e1} = d(U_{e1} - U_{e2} + U_{e2})$   
 $= dU_D + dU_{e2} = dU_D - dU_{e1}$ ,  
thus  $dU_D = \frac{1}{2}dU_{e1}$ .

$\Rightarrow$  Differential amplification  $A_D = \frac{dU_{a1}}{dU_D}$

$$A_D = \frac{dU_{a1}}{2dU_{BE1}} = -\frac{1}{2}S(R_C || r_{CE}).$$

Since  $S$  is large,  $A_D$  is also large.

# Operation of a differential amplifier

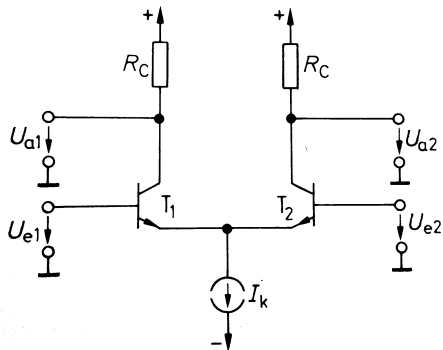

- Constant current source at the emitter.  $\Rightarrow dI_k = 0$ .
- Internal resistance of the constant current source:  $r_k$ .

- $I_k = I_{C1} + I_{C2} \Rightarrow dI_{C1} = -dI_{C2}$ .
- So  $dU_{a1} = -dU_{a2}$ .
- Also  $dU_{e1} = dU_{BE1} = -dU_{BE2} = -dU_{e2}$ .
- $U_D := U_{e1} - U_{e2}$ .  
 $dU_{e1} = d(U_{e1} - U_{e2} + U_{e2})$   
 $= dU_D + dU_{e2} = dU_D - dU_{e1}$ ,  
 thus  $dU_D = \frac{1}{2}dU_{e1}$ .

$\Rightarrow$  Differential amplification  $A_D = \frac{dU_{a1}}{dU_D}$


$$A_D = \frac{dU_{a1}}{2dU_{BE1}} = -\frac{1}{2}S(R_C || r_{CE}).$$

Since  $S$  is large,  $A_D$  is also large.

Besides the differential amplification, there is also a much smaller

**common-mode amplification**  $A_{CM} := \frac{dU_{a1}}{d(U_{e1}+U_{e2})/2} = -\frac{1}{2} \frac{R_C}{r_k}$ , which immediately follows from the formula for the amplification of the emitter circuit with current feedback.

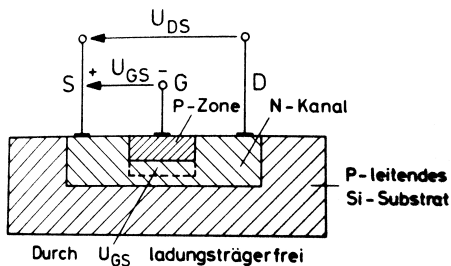
## Construction of an n-channel junction field-effect transistor



S: Source.


G: Gate.

D: Drain.

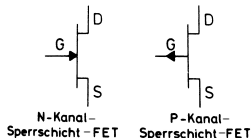

- Control of the size of the charge carrier-free zone via the value of the voltage  $U_{GS}$ .
- Thickness of the charge carrier-free zone determines the resistance between drain and source.
- Advantage of field-effect transistors over bipolar transistors: Lower power consumption, as the control is done via the applied electric field and not via a current.
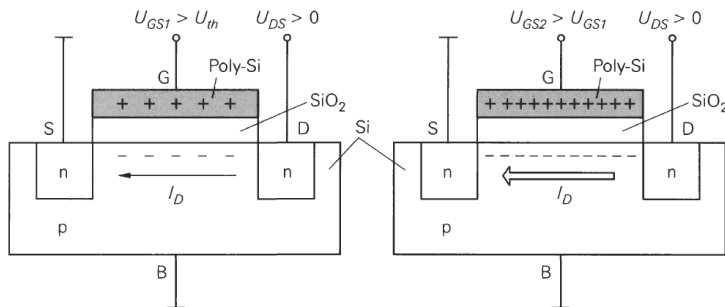
# Metal-oxid-semiconductor field-effect transistor



- Structure forms a capacitor from gate terminal, dielectric, and bulk terminal.
- Application of positive voltage between gate and bulk charges the capacitor.
- Electric field causes migration of minority carriers (electrons in p-silicon) to the junction and recombination with majority carriers (defect electrons in p-silicon), known as “depletion”.
- Space charge region forms at the junction with negative space charge.
- At threshold voltage  $U_{th}$ , displacement of majority carriers becomes significant, limiting recombination.
- Accumulation of minority carriers results in near-inversion of p-doped substrate close to the oxide, known as strong inversion“
- Increased gate voltage induces band bending of conduction and valence bands at the junction in band model.
- Fermi level shifts closer to the conduction band than the valence band, inverting the semiconductor material.
- Formed thin n-type conducting channel connects source and drain n-regions, allowing charge carriers to flow (almost) unimpeded from source to drain.