

INTRODUCTION TO FPGA PROGRAMMING

LESSON 04: SEQUENTIAL LOGIC AND FLIP-FLOPS

Dr. Davide Cieri¹

¹Max-Planck-Institut für Physik, Munich

September 2024

MAX-PLANCK-INSTITUT
FÜR PHYSIK




REMINDER: COMBINATIONAL AND SEQUENTIAL

- A combinational circuit is one whose outputs depend only on the current inputs
- A sequential circuit is one whose outputs depend on the current in inputs and on previous outputs
- On FPGAs sequential logic is achieved using flip-flops or registers


THE CLOCK SIGNAL

 - The *Clock signal* or just *clock*, is a digital signal that alternates between 0 and 1, with a fixed frequency
- Changes in clock signals are called *edges*
 - Rising edge: 0 to 1
 - Falling edge: 1 to 0
- Duty Cycle: fraction of time a clock signal is high



CLOCKS IN AN FPGA

- Clocks inside an FPGA drive all sequential logics (Flip-Flops, RAMs, FIFOs, etc..)
- FPGAs typically support multiple clock domains
 - E.g. different interfaces might require different frequencies, more in another lesson
- Clocks are generated externally to the FPGA and input into special pin
 - Our Basys3 board has an oscillator chip generating a 100 MHz clock, input to pin W5
- A dedicated routing logic is available to minimise skew

 

BASIC TIMING CONSTRAINT

- Your design should know the frequency of the clock you are running
- As all other ports, clocks must be mapped to a physical pin and have a specific IO standard
- All this must be defined in the constraint XDC file


```
set_property PACKAGE_PIN W5 [get_ports CLK]
set_property IOSTANDARD LVCMOS33 [get_ports CLK]
create_clock -period 10.000 -name sys_clk_pin -waveform {0.000 5.000} -add [get_ports
    CLK]
```

create_clock syntax explanation

```
create_clock -period <clock period in ns> \
    -name <a name for your clock> \
    -waveform <optional, otherwise set a half-duty clock by default> \
    -add <map the clock to a specific port>
```



FLIP-FLOPS

 - Flip flops are special circuits used to store state information
- Several types of flip flops can be constructed
 - A good list is available [here](#).
- Most of FPGA vendors employs a D-type Flip-Flop (or *data* flip-flop)



FLIP-FLOP BEHAVIOUR

  - The flip-flop checks the state of the input signal at each rising edge of the clock and set the output (*registering*)



CONCURRENT STATEMENTS IN VHDL

- The `process` statement is used in VHDL to define blocks to be evaluated sequentially
- Statements inside a process are evaluated sequentially (like most programming languages)
- Multiple process blocks are evaluated concurrently

```
<process_name> : process
begin
    statement 1;
    statement 2;
    ...
    statement N;
end process <process_name>;
```

PROCESS SENSITIVITY LIST

- A process can have a sensitivity list
- List of signal to which the process is sensitive (for example a clock)
 - The process is executed only when there is a change to a signal in the sensitivity list

```
<process_name> : process (signalA , signalB)  
begin  
    statement 1;  
    statement 2;  
    ...  
    statement N;  
end process <process_name>;
```

CONDITIONAL STATEMENTS - IF

- `if` statement allows conditional execution inside a `process`
 - Condition should return a boolean
 - Allowed relational operators: Equal(=), Not Equal (/=), Less Than (<), Less Than or Equal to (<=), Greater Than (>), Greater Than or Equal to (>=)

```
if <condition1> then
    <vhdl statement>;
end if;
```

```
if <condition1> then
    <vhdl statement 1>;
else
    <vhdl statement 2>;
end if;
```

```
if <condition1> then
    <vhdl statement 1>;
elsif <condition2> then
    <vhdl statement 2>;
else
    <vhdl statement 3>;
end if;
```

CONDITIONAL STATEMENTS - CASE

```
case <signal> is
  when <condition A> => <statement A>;
  when <condition B> => <statement B>;
  when others => <statement C>;
end case;
```

- Similar to switch in C
- Default option `others` is available
- `null` is a valid VHDL statement that can be used if no assignment is wanted

CONDITIONAL STATEMENTS - EXAMPLES

```
process(a,b,sel)
begin
  if sel = '0' then
    y <= a;
  elsif sel = '1' then
    y <= b;
  else
    null;
  end if;
end process;
```

```
process(a,b,sel)
begin
  case sel is
    when '0' => y <= a;
    when '1' => y <= b;
    when others => null;
  end case;
end process;
```

EDGE DETECTION IN VHDL

- The `ieee.std_logic_1164.all` package contains useful functions to detect signal (and clock) edges
 - `rising_edge(s)` returns `true`, if there is a rising edge on the signal `s`
 - `falling_edge(s)` returns `true`, if there is a falling edge on the signal `s`

```
-- A D-Flip-Flop implementation
process (clk)
begin
    if rising_edge(clk) then
        Q <= D;
    end if;
end process;
```

UNDERSTANDING SIGNAL ASSIGNMENTS IN VHDL PROCESSES

- Statements within a VHDL process are executed sequentially.
- However, signal assignments take effect only at the end of the process.
- Risk: Overwriting earlier assignments within the same process.
 - Example: Flip-Flop driven by multiple inputs within a single clock cycle.

```
process (clk) is
begin
    if rising_edge (clk) then
        a <= b; -- Overwritten by later assignments
        b <= c;
        c <= a;
        a <= c; -- This is the final assignment to 'a'
    end if;
end process;
```

RESETS


- Two types of resets can be defined.
 - Asynchronous Reset. Reset signal is not synchronous to the process clock.
 - Synchronous Reset. Reset signal is synchronous to the process clock.

```
-- D-Flip-Flop with Asynchronous Reset
process (clk, rst)
begin
  if rst = '1' then
    Q <= '0';
  elsif rising_edge(clk) then
    Q <= D;
  end if;
end process;
```


```
-- D-Flip-Flop with Synchronous Reset
process (clk)
begin
  if rising_edge(clk) then
    if rst = '1' then
      Q <= '0';
    else
      Q <= D;
    end if;
  end if;
end process;
```


RESETS

 - Two types of resets can be defined.
 - Asynchronous Reset. Reset signal is not synchronous to the process clock.
 - Synchronous Reset. Reset signal is synchronous to the process clock.




Asynchronous Reset

 

Synchronous Reset

SHIFT REGISTERS

 

- A cascade of flip-flops where the output of one flip-flop is connected to the input of the next, is called **Shift Register**.
- Very useful module, for deserialization and pipelining

SHIFT REGISTERS IN VHDL

```
process (clk)
begin
    if rising_edge (clk) then
        Q(3 downto 1) <= Q(2 downto 0);
        Q(0) <= D;
    end if;
end process;
```

CONSTANTS

- As in common programmable languages, it is possible to define constants in VHDL
 - Improve code readability
 - If used in multiple places, only one change needed. Improved code maintenance
 - Can be defined in `process`, `architecture` or `package` blocks

```
architecture RTL of MyModule is
    constant SIGNAL_WIDTH : integer := 16;
    signal my_signal : std_logic_vector(
        SIGNAL_WIDTH-1 downto 0);
begin
    ...
end architecture RTL;
```

```
process (clk)
    constant reset_value :
        std_logic_vector := "1010";
begin
    if rising_edge (clk) then
        if mysignal = reset_value then
            mysignal <= (others => '0');
        end if;
    end if;
end process;
```

VARIABLES

- Variables are VHDL objects local to a VHDL process
 - They cannot be used outside the process, where they are defined
- They can be of any type
- Value assignment using the `:=` symbol
- Variables take immediately the value of the assignment

```
EXAMPLE_VAR : process (clk)
  variable v_Count : integer := 0;
begin
  if rising_edge(clk) then
    -- Assume v_Count is 4
    v_Count := v_Count + 1; -- v_Count updates to 5
    r_Var_Copy1 <= v_Count; -- r_Var_Copy2 updates to 5 the next clock cycle
    if v_Count = 5 then
      v_Count := 0; -- v_Count updates to 0 immediately
    end if;
    r_Var_Copy2 <= v_Count; -- r_Var_Copy2 updates to 0 the next clock cycle
  end if;
end process EX_VAR;
```

WHILE STATEMENT

- **Syntax:**

```
while <condition> loop
  <sequential statements>
end loop;
```

- **Description:**

- Repeats a block of code as long as the condition is true.
- The condition is evaluated before each iteration.
- Used for loops where the number of iterations is not known beforehand.

- **Example:**

```
process
  variable i : integer := 0;
begin
  while i < 10 loop
    -- Perform some operation
    i := i + 1;
  end loop;
end process;
```

FOR STATEMENT IN VHDL

- **Syntax:**

```
for <loop_variable> in <range> loop
    <sequential statements>
end loop;
```

- **Description:**

- Repeats a block of code a fixed number of times.
- The loop variable automatically iterates over the specified range.
- Used when the number of iterations is known beforehand.

- **Example:**

```
process
begin
    for i in 0 to 9 loop
        -- Perform some operation
    end loop;
end process;
```

LAB 07: COUNTERS AND DEBOUNCING

LAB 08: AN LED BLINKER

The figures in these slides are taken from:

- Digital Design: Principles and Practices, Fourth Edition, John F. Wakerly, ISBN 0-13- 186389-4.

©2006, Pearson Education, Inc, Upper Saddle River, NJ. All rights reserved

- nandland.com

- docs.amd.com

- <https://www.symmetryelectronics.com/>

- <https://www.edn.com/>