INTRODUCTION TO FPGA PROGRAMMING

LESSON 09A: THE 7-SEGMENT DISPLAY

Dr. Davide Cieri¹

¹Max-Planck-Institut für Physik, Munich

September 2024



INTRODUCTION TO THE 7-SEGMENT DISPLAY

- The Basys 3 board has one 7-segment displays with four digits.
- Each digit composed by seven segments arranged in a figure 8 pattern, with an LED embedded in each segment.
 - Segments can be individually illuminated
 - 128 possible patterns, including 10 for decimal digits



7-SEGMENT DISPLAY BASICS

- One common anode for all the seven LEDs forming a digit
- Cathodes are separated for each segment, to allow individual activation.
- Cathodes are common for all four digits.
 - CA-CG plus DP for the points.



HOW TO ILLUMINATE A SEGMENT?

- To illuminate a segment, you should drive the anode input of the chosen digit low.
- Also set low the signals for the chosen segment cathodes, to illuminate the segment.
- Since, the human eye can not detect rate faster than 45 Hz, you can implement a circuit (FSM) that updates the value of digits one at the time.



HOW TO ILLUMINATE A SEGMENT?

- For each digits to appear continuously illuminated, they all should be driven once every 1 to 16ms, for a refresh frequency of about 1KHz to 60Hz.
- For example, in a 62.5Hz refresh scheme, the entire display would be refreshed once every 16ms, and each digit would be illuminated for 1/4 of the refresh cycle, or 4ms.



LAB 15: DESIGN A STOP WATCH

The figures in these slides are taken from:

- Digital Design: Principles and Practices, Fourth Edition, John F. Wakerly, ISBN 0-13- 186389-4. ©2006, Pearson Education, Inc, Upper Saddle River, NJ. All rights reserved

- allaboutfpga.com
- nandland.com
- docs.amd.com
- https://www.symmetryelectronics.com/
- https://www.edn.com/
- Stephen A. Edwards, Columbia University, Fundamentals of Computer Systems, Spring 2012
- https://medium.com/well-red/state-machines-for-everyone-part-1-introduction-b7ac9aaf482e