



DEPFET System Simulation



Jochen Knopf

jochen.knopf@ziti.uni-heidelberg.de

BELLE II PXD / DEPFET Meeting

Prague

26.01.2010

- Motivation
- DEPFET System Simulation Environment
- Simulation Examples
- Open Issues


Motivation

The DEPFET PXD front-end electronics consist of:


- DEPFET Matrix (HLL Munich)
- SwitcherB (Uni Heidelberg)
- DCDB (Uni Heidelberg)
- DHP (Uni Bonn)
- DHH (Uni Göttingen)

Each chip is designed and tested separately.
Do they work together?

A Simulation can give the answer!

 


DEPFET System Simulation Environment

 


- The Simulation includes Models of the SwitcherB, the DCDB and the DEPFET Matrix.
- The Testbench stimulates the SwitcherB and the DCD
- The SwitcherB steers the DEPFET Matrix
- The DCDB reads the DEPFET Matrix


Simulation Details: The DEPFET Model

 

- 3 Pixel Matrix (3 Rows, 1 Column)
- RC lines for gate, clear and drain wires
 - Gate: ΣR 40 Ω , ΣC 50pF
 - Clear: ΣR 40 Ω , ΣC 50pF
 - Drain: ΣR 300 Ω , ΣC 50pF
- Matrix Model: Spectre Netlist
- Transistor Model: SpectreCMI (Ref.: A. Wassatsch, Ringberg, May 2009)

Simulation Details: The SwitcherB Model

 

 


- Included Blocks
 - Single instance of DCDB's analog ADC pixel (Spectre Netlist)
 - Entire digital block (Verilog)
- Transistor Models: UMC CMOS 180nm

- The simulation environment consists of
 - Verilog files (DCDB digital block, stimulus generator,...)
 - VerilogAMS files (Testbench,...)
 - Spectre netlist files (DCDB analog pixel, SwitcherB output driver)
 - UMC 180nm 1P6M MM/RFCMOS transistor models (DCDB analog pixel)
 - AMS 350nm HV CMOS transistor models (SwitcherB output driver)
 - HLL DEPFET model, written in SpectreCMI
- Simulation Software: Cadence Incisive Unified Simulator 9.2
 - Analog simulator: Spectre
 - Digital simulator: NCSim


→ We are exhaustively using cutting-edge simulation technology!

Simulation Examples


- Supply voltages
 - Matrix source: 5.74V (rel. to ground)
 - Clear voltages (rel. to matrix source potential)
 - Clear-Low: 0V
 - Clear-High: 13V
 - Gate voltages (rel. to matrix source potential)
 - Gate-Low: -3.24V
 - Gate-High: 6.76V
 - SwitcherB supply voltage: 3.3V (rel. to ground)
 - DCDB supply voltage: 1.8V (rel. to ground)
- Scenario
 - Scanning through the Matrix in a rolling shutter mode
 - DCDB operates in single sampling mode, ~50uA pedestal subtraction
 - SwitcherB settings:
 - Gate pulse width: 320ns
 - Clear pulse of 40ns at the end of a gate pulse
 - Matrix settings:
 - Pixel 0 and 2 are initially loaded (→ signal!)
 - Pixel 1 initially unloaded (→ no signal!)

 

Simulation Example: Screenshot

 

 Simulation Example: Clear Pulse Width vs. Signal Amplitude



Open Issues

1. Get more realistic models

- DCDB, SwitcherB: Use RC-extracted Spectre netlists
- DEPFET Matrix: Include coupling caps between transistor terminals, ...
- Extract RC of the chip interconnections

→ Need simulation performance

2. Fight simulation software bugs

- Finding / exploring bugs
- Developing work-arounds


→ Need several runs for debugging (performance!)

3. Solve simulation performance issues

- Suitable hardware infrastructure is available:
2x Quad-Core Intel Xeon 3GHz CPU with 32GB RAM
- Simulation runs on only two threads, one for each simulator
(CPU usage: ~140%)

→ Possible solution: Cadence Accellerated Parallel Simulator (APS)

 - We have the licences
- Used routinely by us for analog and mixed-signal simulations
- Measured: CPU usage constantly 400-600%
- The SpectreCMI model of the DEPFET transistors is not ready to support APS



- The DEPFET system simulation environment is set up and running!
 - Included models:
 - SwitcherB
 - DCDB
 - DEPFET Matrix
 - There are still some open issues
- We have a powerful tool for checking the correct chip interaction!

Thank you!