

# Some experience with ST radhard voltage regulators LHC4913 and LHC7913

## Distributed low voltage power supply system for front end electronics of the TRT detector in ATLAS experiment

Hajduk, Z ; [Banas, E](#) ; [Farthouat, P](#) ; [Kisielewski, B](#) ; [Lichard, P](#) ; [Olszowska, J](#) ; [Ryzhov, V](#) ; [Cardiel-Sas, L](#)

Henryk Niewodniczański Institute of Nuclear Physics PAN, Cracow, Poland  
; CERN    [12th Workshop on Electronics For LHC and Future Experiments](#),  
Valencia, Spain, 25 – 29,2006

### 1. Experiences from ATLAS

- Remote sensing
- Remote adjustment of output voltage
- Monitoring of output voltage and current
- Parallel connection of voltage regulators



### 2. Considerations for DEPFET




# Low Voltage Power Supply system of the TRT detector in ATLAS



1408 FEE cards

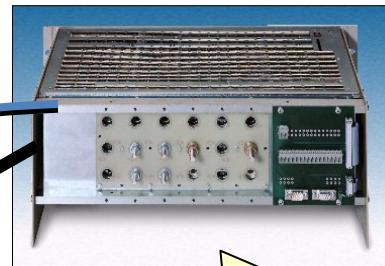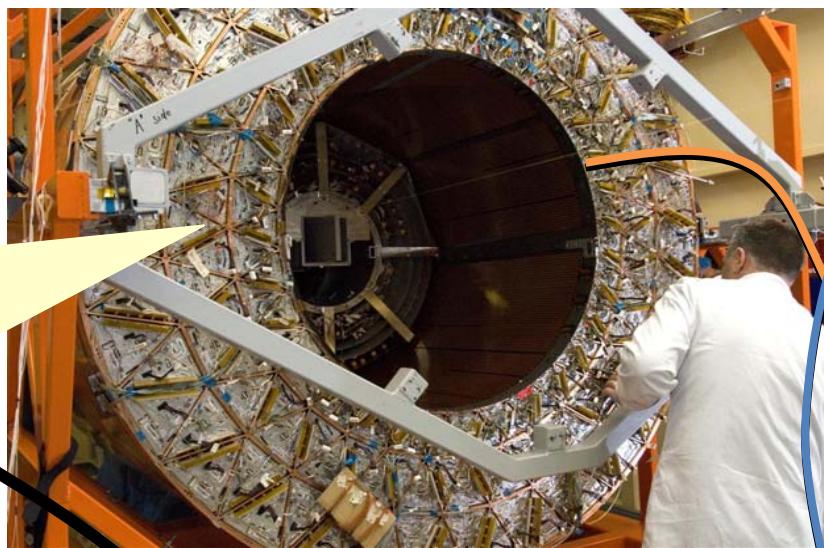

Bulk Low Voltage Power Supply

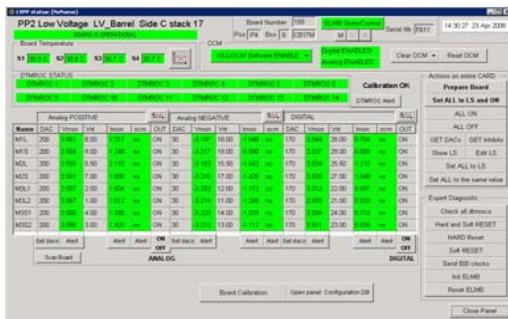

24 or 36 LHC4913 and LHC7913

Voltage regulators


+2.5 V, +3.0 V, -3.0 V

4224 low voltages

80 m



15 X 36 cm

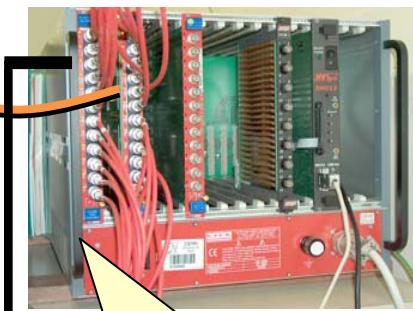


High Voltage Power Supply




KVASER  
interface PCI – CAN

PCI

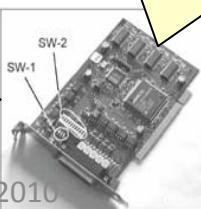

CAN

192 LVPP



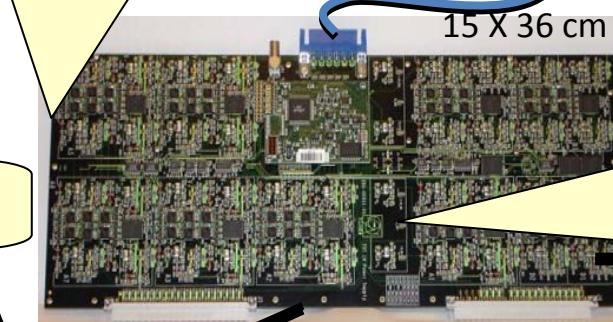


ELMB



Embedded Local Monitor Board





# Remote sensing 20 m / 370 mOhm

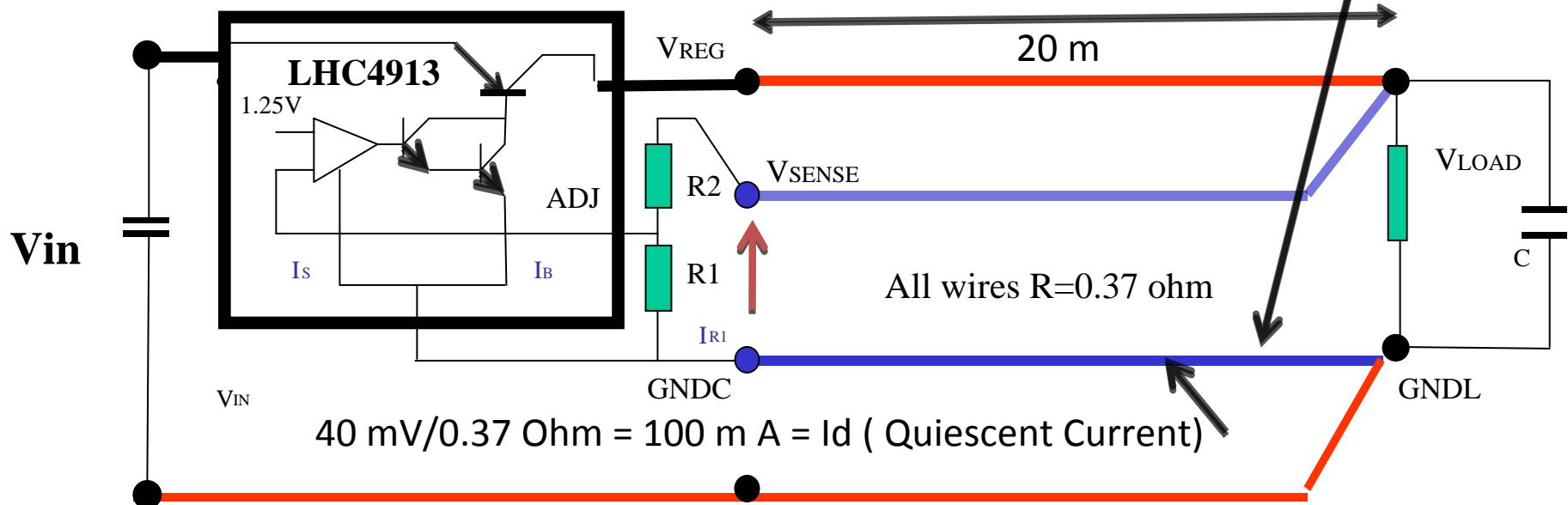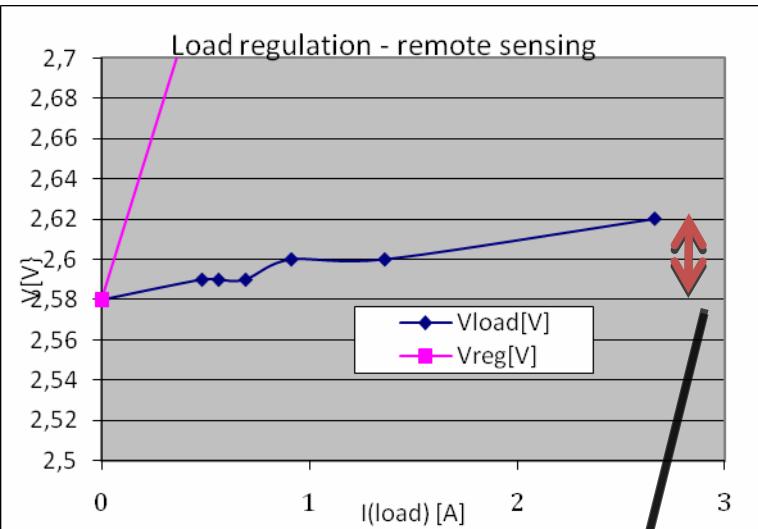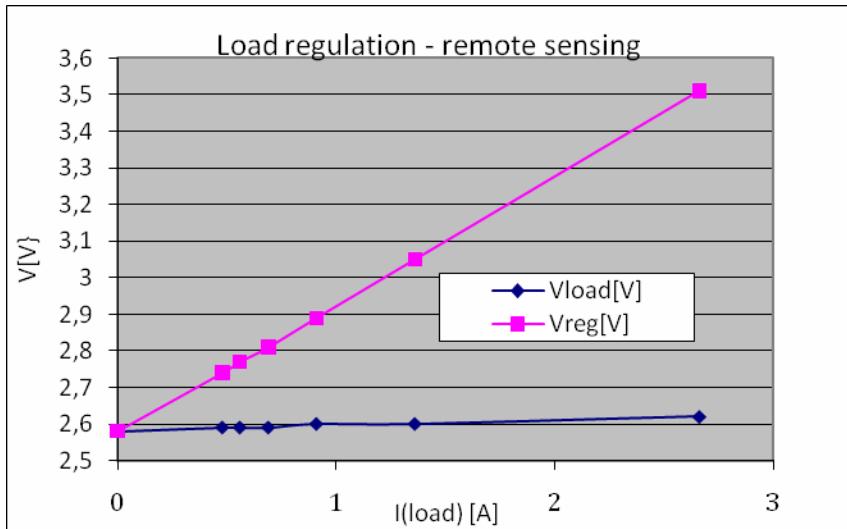

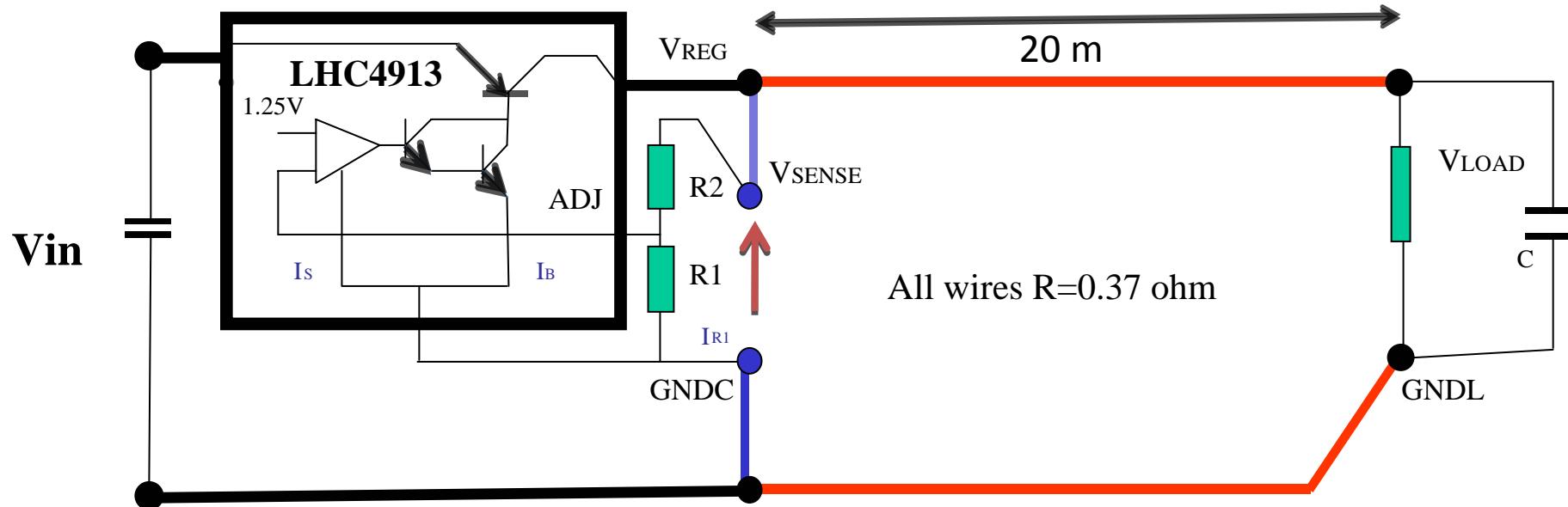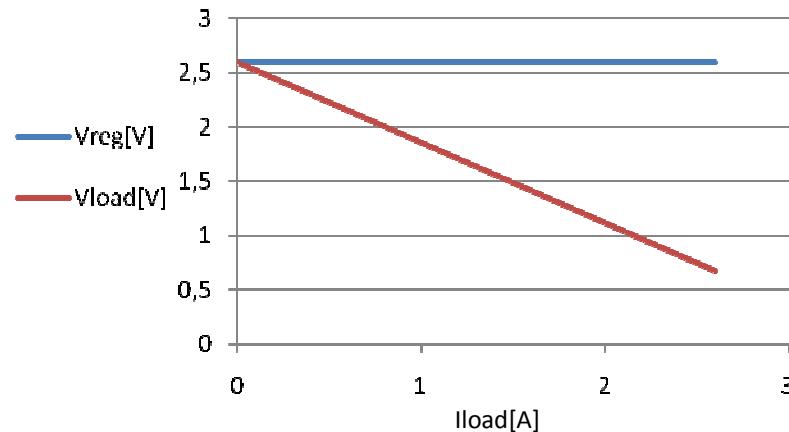
## Without Remote sensing 20 m / 370 mOhm




# Remote adjustment of output voltage

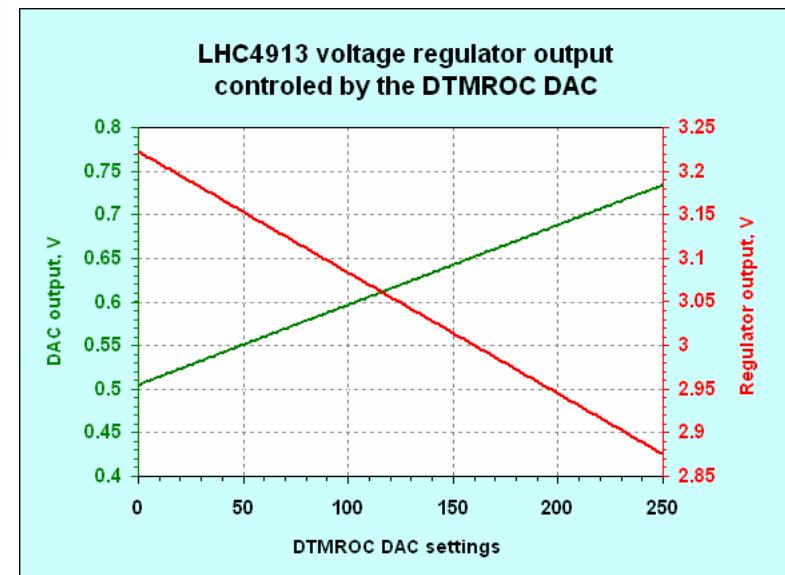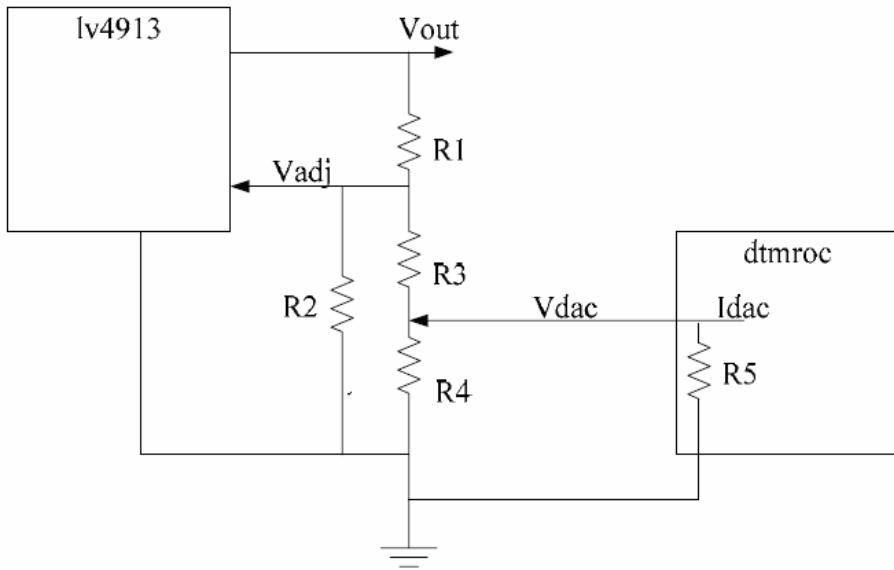
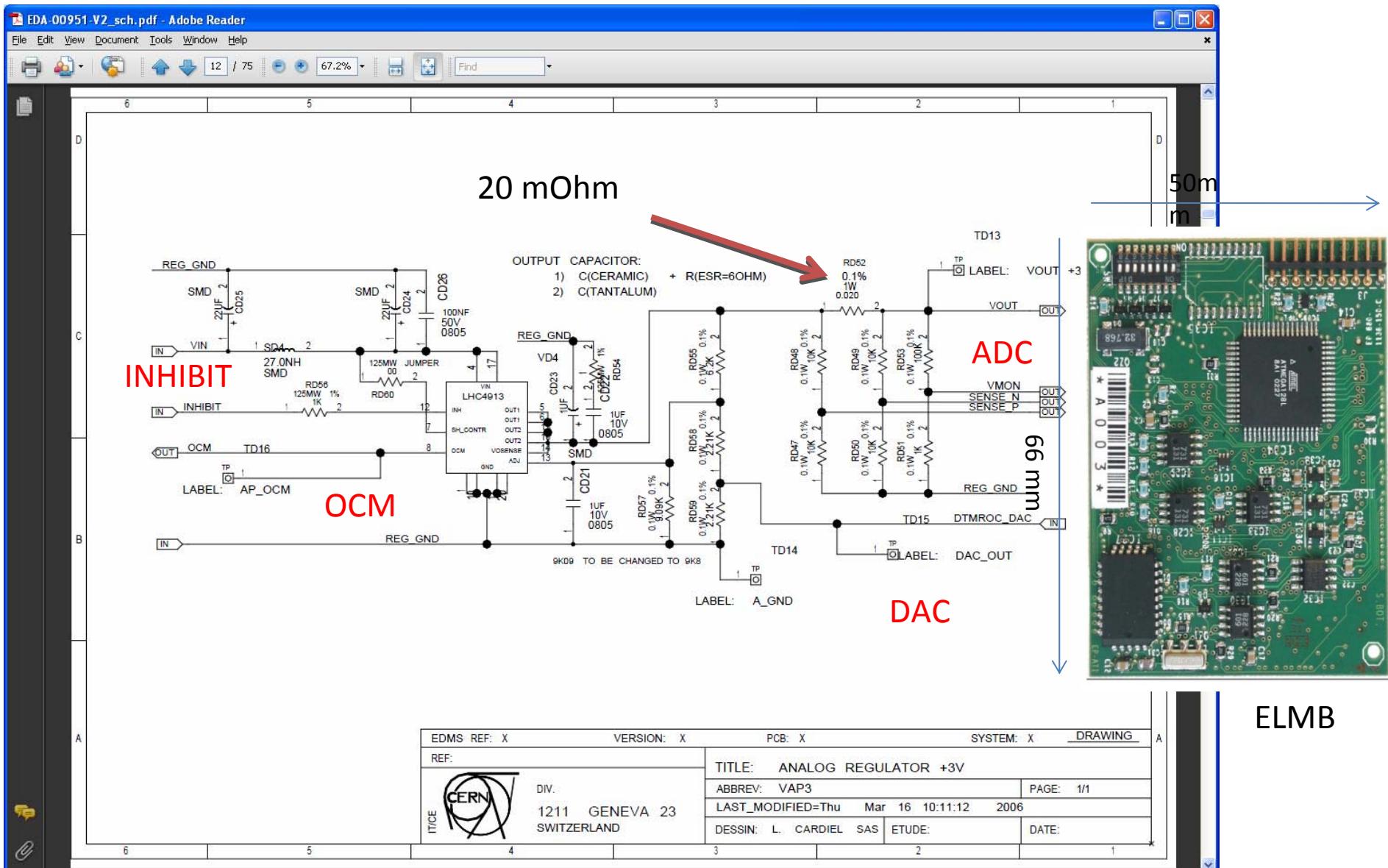
# Voltage and current monitoring of voltage regulator


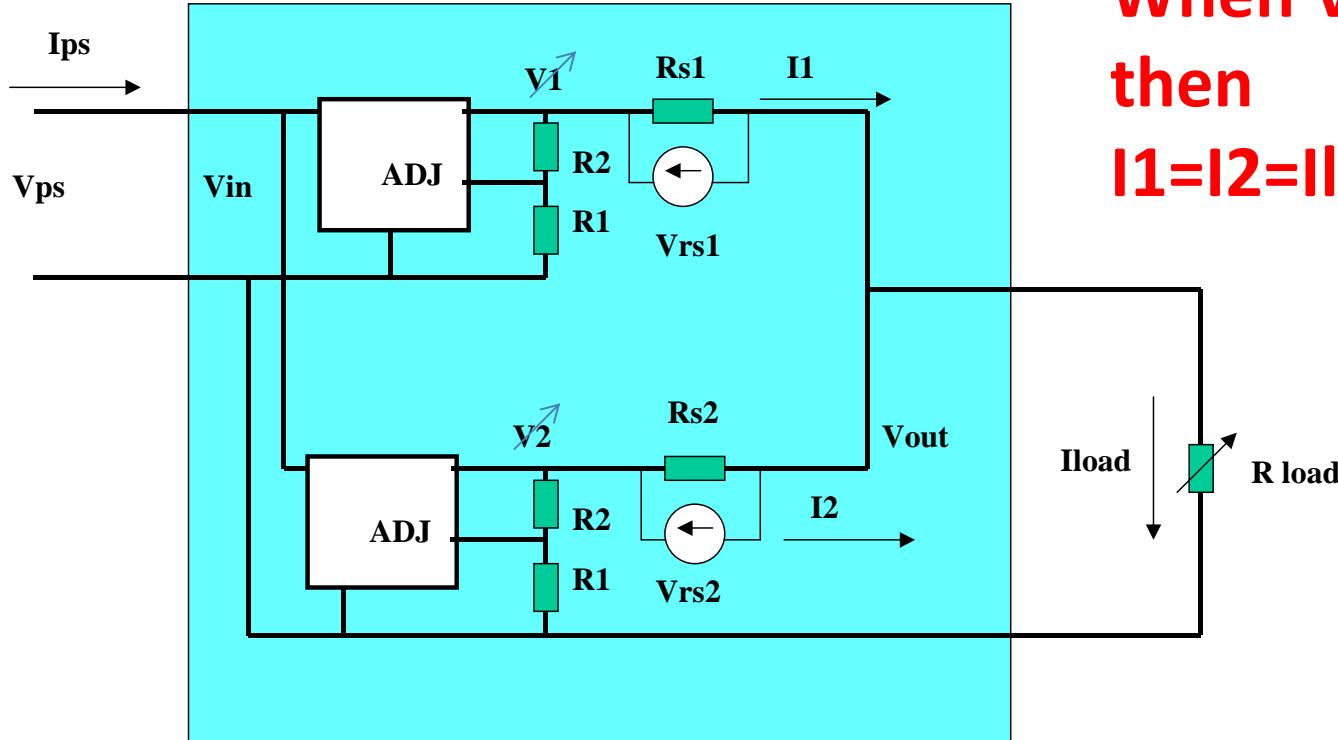
# Parallel connection of voltage regulators



When  $V_1=V_2$   
then  
 $I_1=I_2=I_{load}/2$

$$V_{rs1}=V_{rs2}=20 \text{ mOhm} * 1.15A = 23 \text{ mV}$$

http://stukieles.home.cern.ch/stukieles/LHC4913.pdf - Windows Internet Explorer

File Edit Przyjdź do Usługi Pomoc Google

http://stukieles.home.cern.ch/stukieles/LHC4913.pdf

Search WINAMP


Przeglądarka Internetowa

LHC4913 SERIES  
3A POSITIVE LOW DROP VOLTAGE REGULATOR WITH INHIBIT FUNCTION

- LOW OUTPUT CAPACITANCE:  $1\mu F$
- LOW DROP VOLTAGE:  
 $0.5V @ I_o=1A$   
 $1.5V @ I_o=3A$
- OVERTEMPERATURE PROTECTION
- OVERCURRENT PROTECTION
- OUTPUT SHORT CIRCUIT MONITORING, SIGNALLED BY TTL OUTPUT
- ON/OFF EXTERNAL CONTROL BY MEANS OF TTL COMPATIBLE INPUT
- ADJUSTABLE CURRENT LIMITATION PROTECTS OUTPUTS FROM DAMAGING SHORTCIRCUITS
- REMOTE SENSING OPERATION

PowerSO-20 slug-up

# Radhard Voltage Regulators from ST

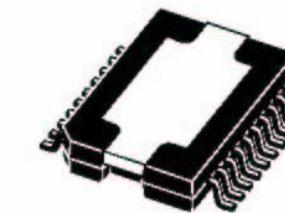

PowerSO-20 (Slug-up)

rhfl4913a.pdf - Adobe Reader

File Edit View Document Tools Window Help


1 / 20 140% Find

RHFL4913A

Rad-hard adjustable positive voltage regulator
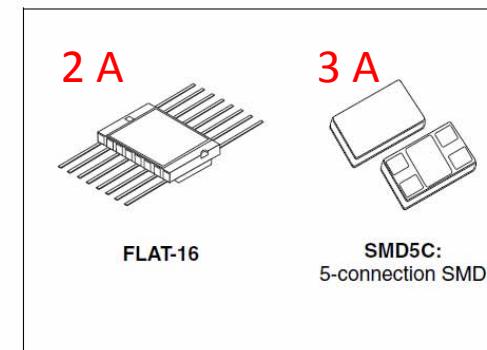
## Features

- 3 A low dropout voltage
- Embedded overtemperature and overcurrent protection
- Adjustable overcurrent limitation
- Output overload monitoring/signalling
- Adjustable output voltage
- Inhibit (ON/OFF) TTL-compatible control
- Programmable output short-circuit current
- Remote sensing operation






2A	3A
Vout	Vout
Vin	Vin
GND	GND
Isc	
OCM	
Inhibit	Inhibit
ADJ	ADJ

## Survey of radhard voltage regulators


www		Type	Package	Vo [V]	Io [A]	ADJ	Inhibit	OCM	Ishort	RAD-hard
1 <a href="http://www.st.com">www.st.com</a>	ST	LHC4913	SO20 slug-up	1.23 - 9	3	x	x	x	x	1 Mrad
2 <a href="http://www.st.com">www.st.com</a>	ST	RHFL4913A	FLAT-16	1.23 - 9	2	x	x	x	x	300 krad
3 <a href="http://www.st.com">www.st.com</a>	ST	RHFL4913A	SMD5C	1.23 - 9	3	x	x			300 krad
4 <a href="http://www.mskenedy.com">www.mskenedy.com</a>	MSK	5800RH	SMP	1.5 - 6.8	4	x	x			450 krad
5 <a href="http://www.linear.com">www.linear.com</a>	LINEAR International	RH1085	K PACKAGE	1.22- 25	3	x				200 krad
6 <a href="http://www.irf.com">www.irf.com</a>	Rectifier	IRUH33P183B1M	MO-078AA		1.8	3	Fixed	x		1 Mrad
7	Linfinity	SGGR117A (LM117A)	TO-257(TO-220)	1.22 - 37	1.5	x				1 Mrad
8 <a href="http://www.aeroflex.com/voltreg">www.aeroflex.com/voltreg</a>	Aeroflex	VRG8691/92	Hermetic metal	1.0 - 3.3	7.5	x	x			100 krad
9 <a href="http://www.intersil.com">www.intersil.com</a>	intersil	HS-117RH	SMD.5/TO-257	1.2 - 37	1.25	x				300 krad

Nr	short name	name	V	$\Delta V$	$I_{max}$	comment
0	common	common digital power				
0.1	DVDD 1.8	DVDD DCD, JTAG SW, DVDD IO DHP	1.8		1000mA	
0.1.1	sDVDD 1.8	sense DVDD 1.8				
0.2	DGND	comon digital ground	0		1400mA	
0.2.1	sDGND	sense DGND				
1	DCD	DCD power				
1.1	AVDD DCD	DCD analog supply	1.8V	?	2.3A	-
1.1.1	sAVDD DCD	sense line AVDD DCD				
1.2	AGND DCD	DCD analog ground	0	?	-2.3A	-
1.2.1	sAGND DCD	sense line AGND DCD				
1.3	REFIN DCD	ref.of mem cell	1.1V	?	200 mA	-
1.4	AmpLow	analog ground for amp.		?		
2	SW	switcher power				
2.1	DVDD SW	switcher digital supply	3.3V	?	4mA	-
2.1.1	sDVDD SW	sense of DVDD SW				-
2.2	CLEAR on SW	clear on	17V	?	27mA	-
2.3	CLEAR off SW	clear off	8V	?	-27mA	-
2.4	sub	substrate	lowest			local?
2.5	GATE on SW	gate on	4V	?	27mA	-
2.6	GATE off SW	gate off	13V	?	27mA	-
3	DHP	DHP power				
3.1	DVDD DHPCORE	DHP digital supply	1V	?	500mA?	-
3.1.1	sDVDD DHP	sense of DVDD DHPCORE				
3.2	DVDD DHPGP	supply for gigabit link	1.2V			
4	DEPFET	DEPFET sensor				
4.1	VSOURCE	source	7V		100mA	
4.2	VCCG	common clear gate	7V			
4.3	VBULK	bulk	17V			
4.3	VBP	back plane	-20V			
4.4	VGUARD	guard ring				

Table 1.1: Power lines per module

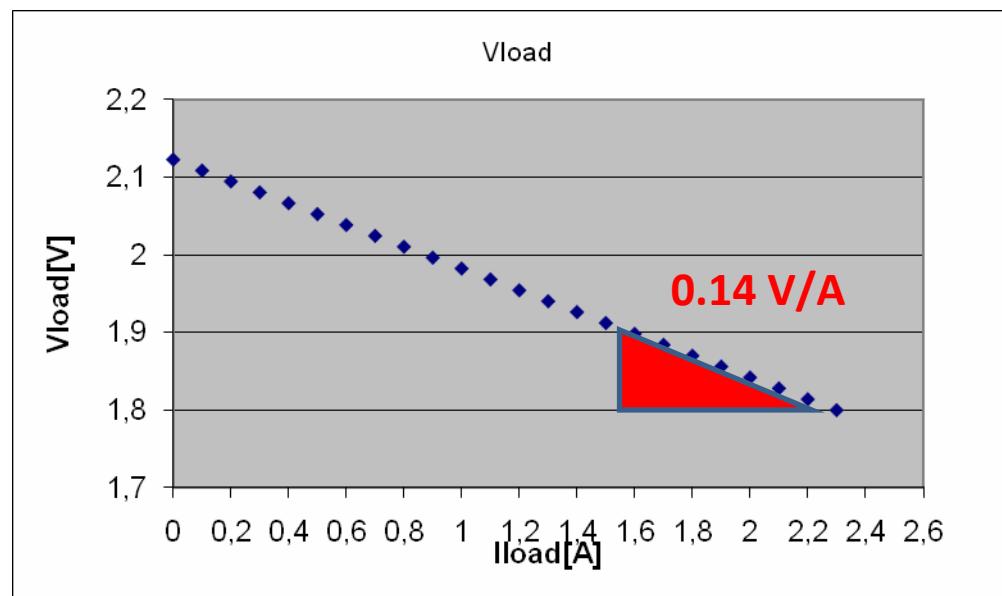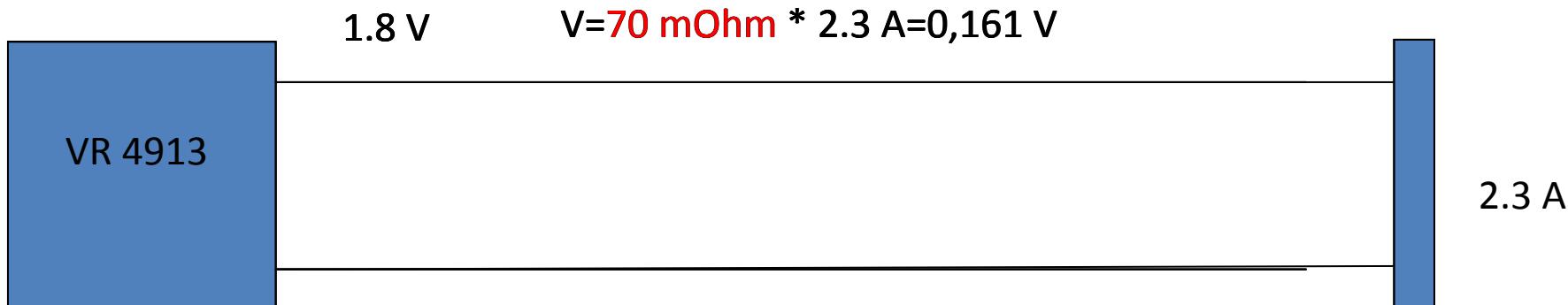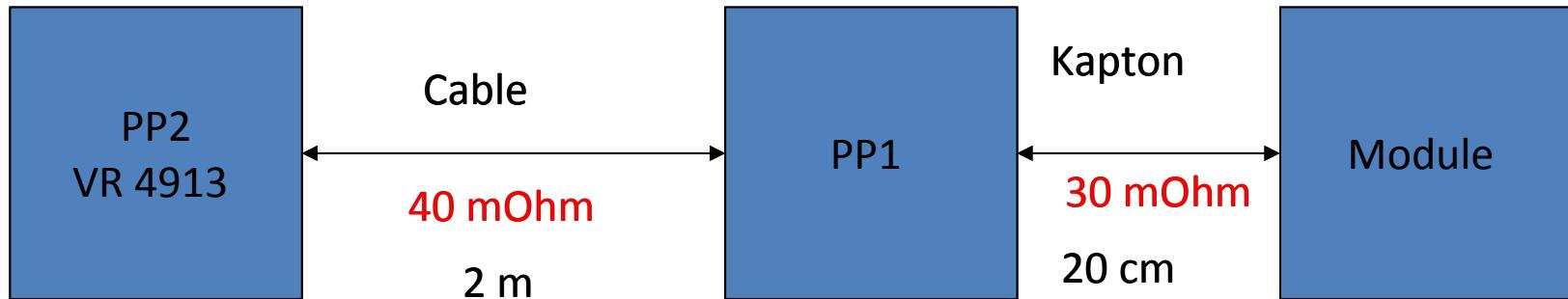


# Remote sensing

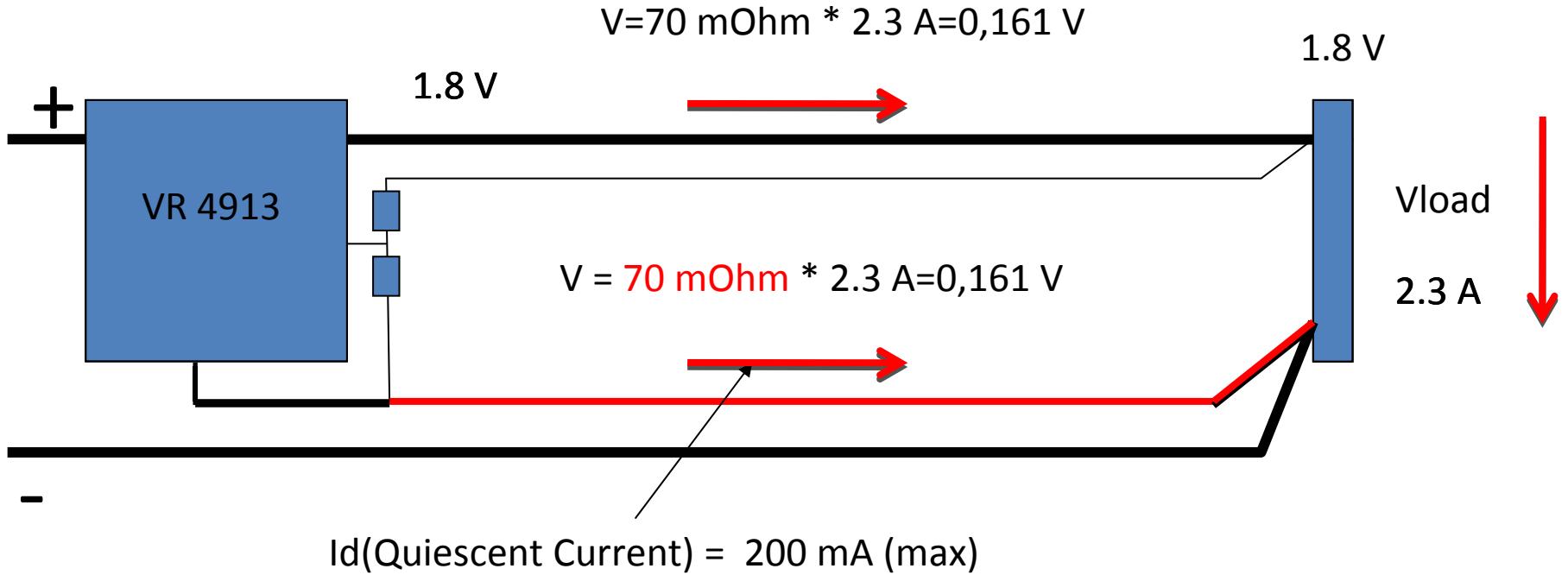

$$V_{sense} = 0.2 \text{ A} * 0.070 \text{ Ohm} = 0.014 \text{ V} = 14 \text{ mV}$$

$$V_{cense} = 0.2 \text{ A} * 0.120 \text{ Ohm} = 0.024 \text{ V} = 24 \text{ mV}$$

## Remote sensing - 220 cm/ 70 mOhm

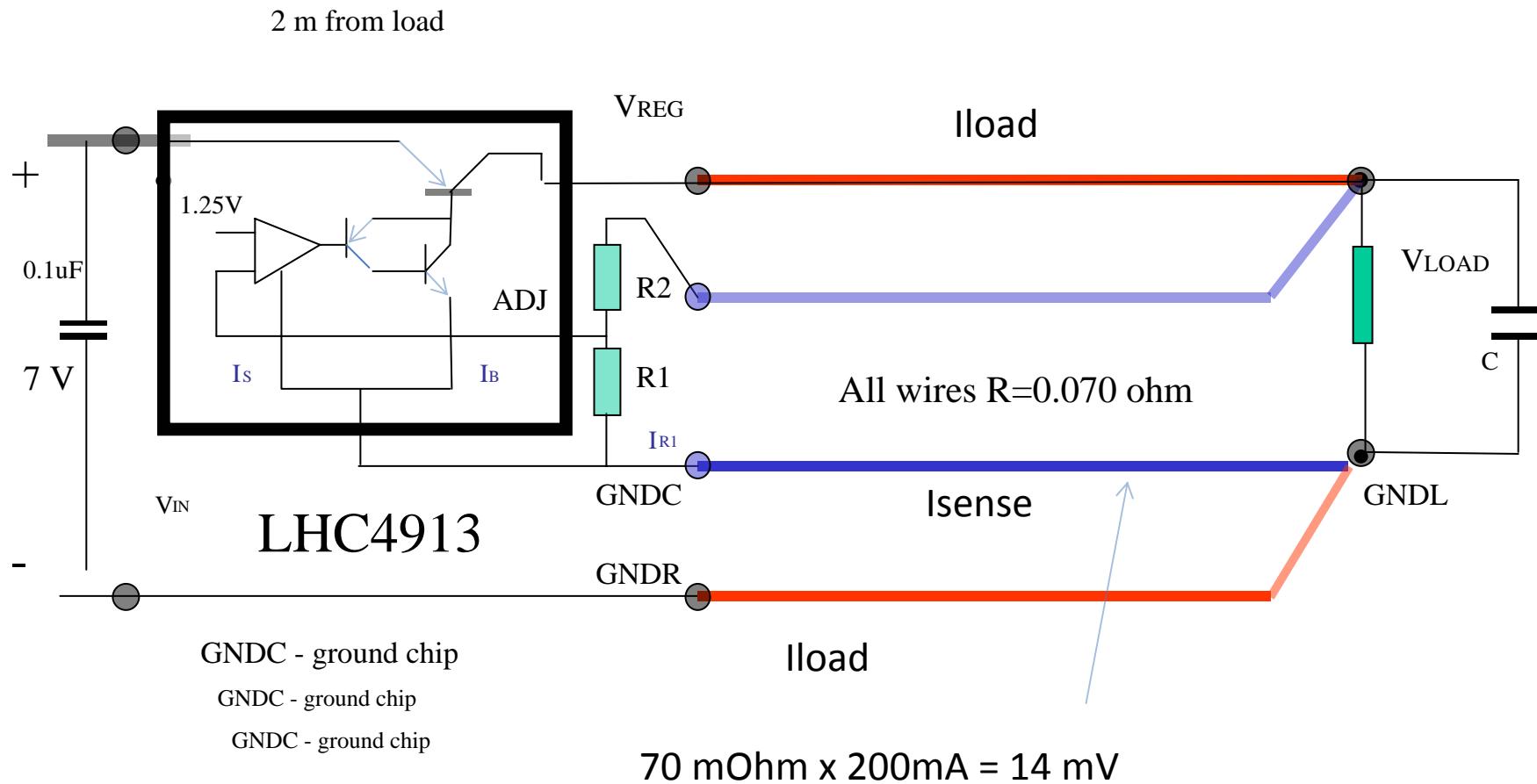


# Load and line regulation



$V_b$  10-20 m  
 $V_{in}$   
 $I = I_1 + I_2 + I_3 + I_4$

**Line regulation**

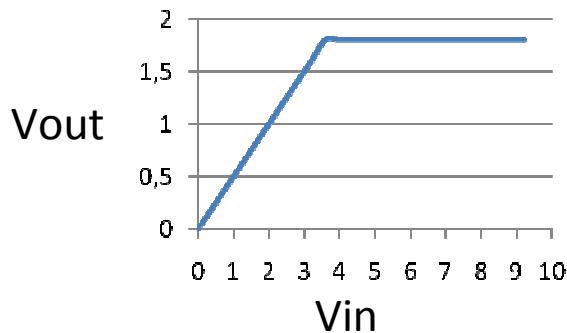

**Load regulation**

