



Switcher-B



Christian Kreidl

christian.kreidl@ziti.uni-heidelberg.de


5th International Workshop on DEPFET Detectors

and Applications


Valencia

 29.09 – 01.10.2010


- 32 rows
 - each row with clear and gate output
 - shift register to enable rows (LVDS)
 - gate and clear strobe signals (LVDS)
 - sleep and boost states for power saving
- AMS H35B4 technology
- radiation hard design
- floating digital 3.3V supply
- JTAG slow control and boundary scan
 - 1.8V capable I/Os
- bump bond only
- designed size: 2100 μm x 3600 μm
- measured size: 2170 μm x 3660 μm
- see Reference Manual for more details!





Chip Layout

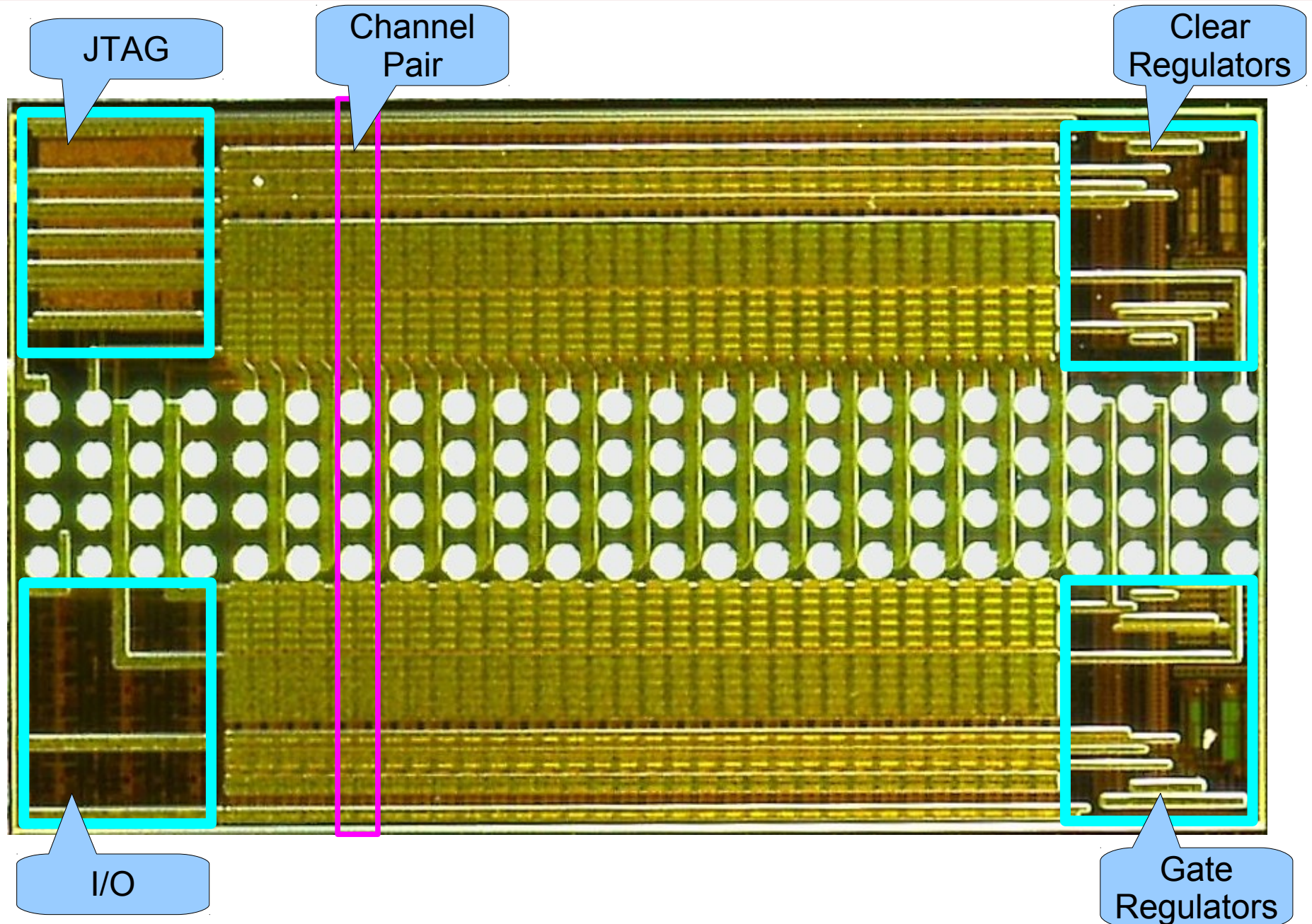

Blockdiagram JTAG

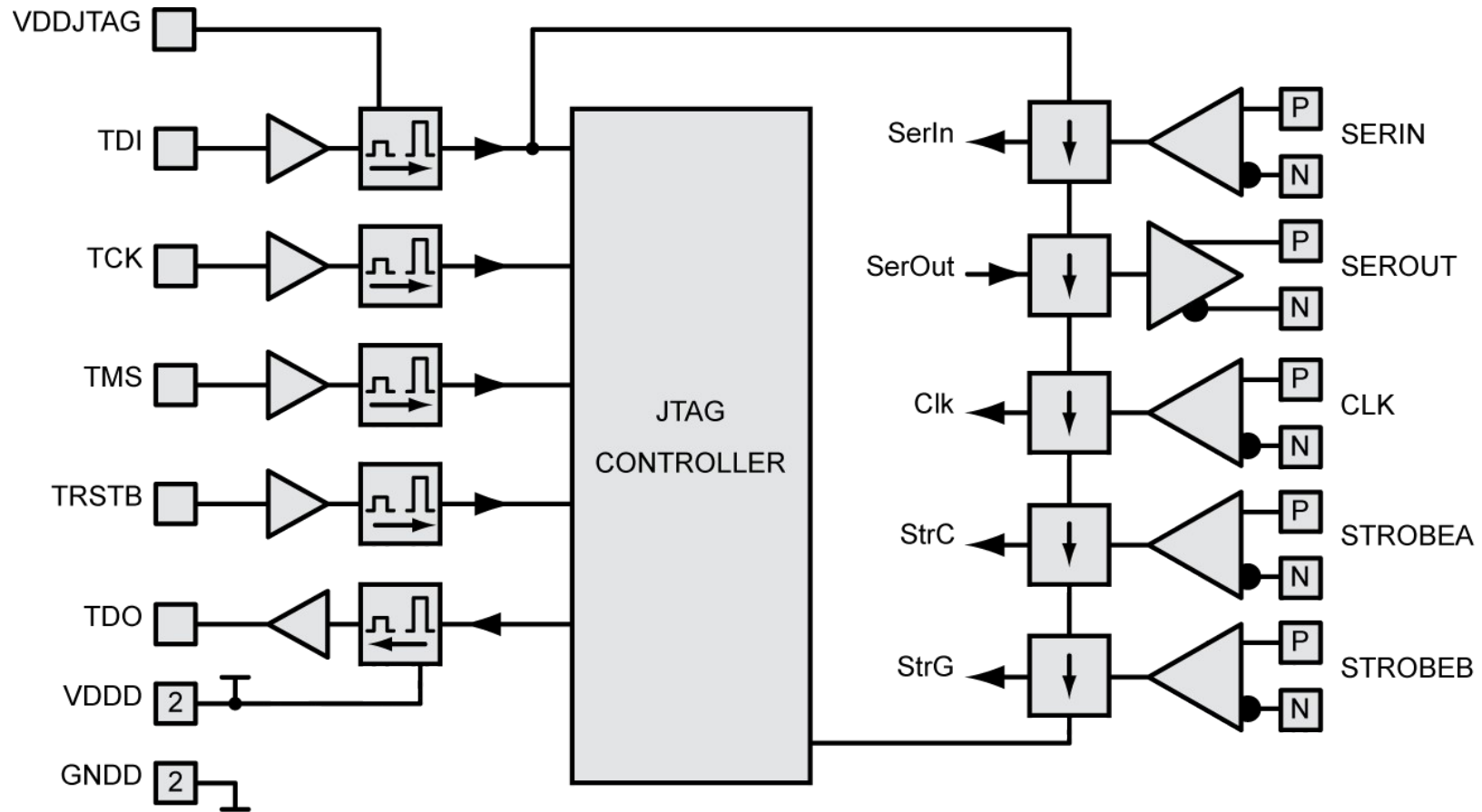


Blockdiagram Switches

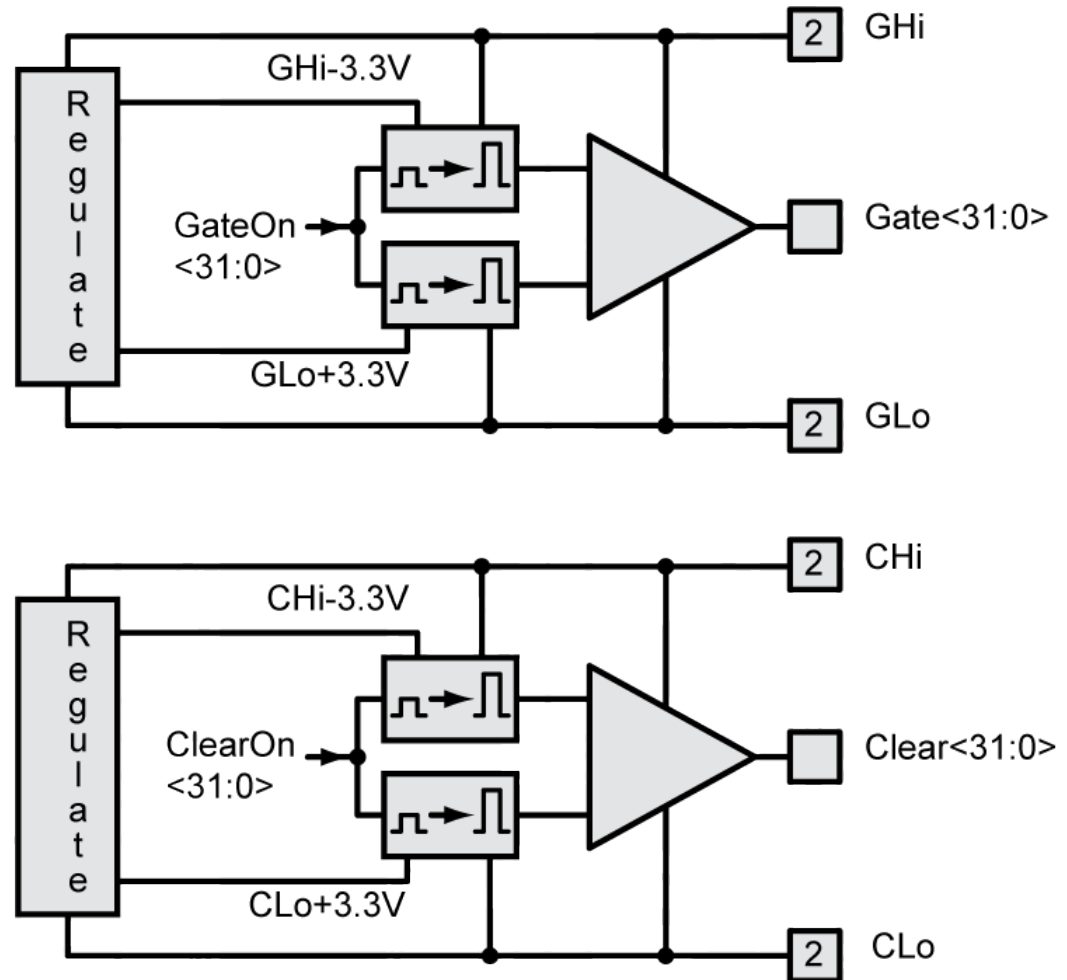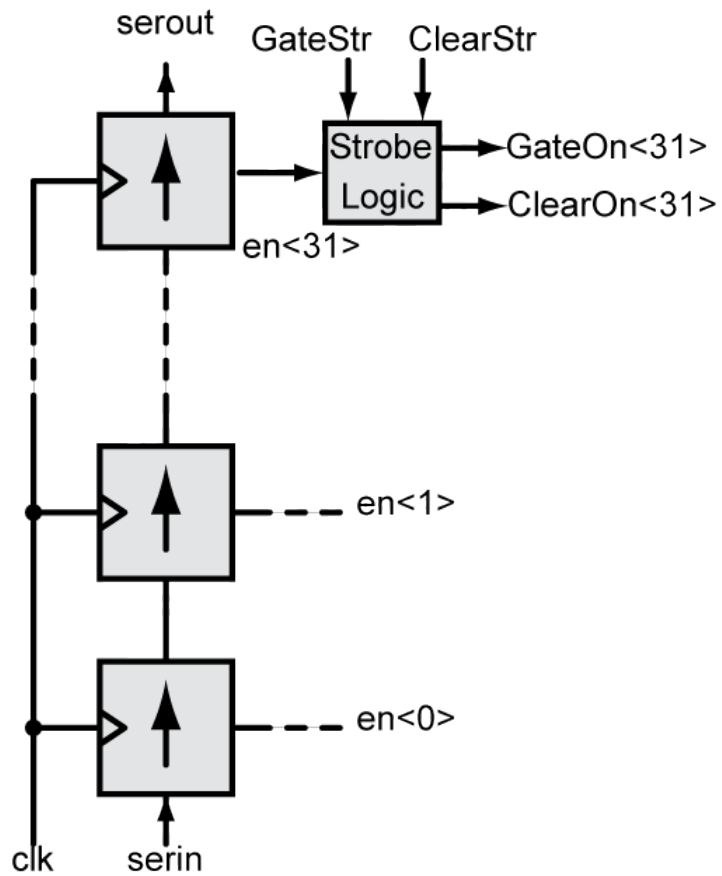

Supply Voltages

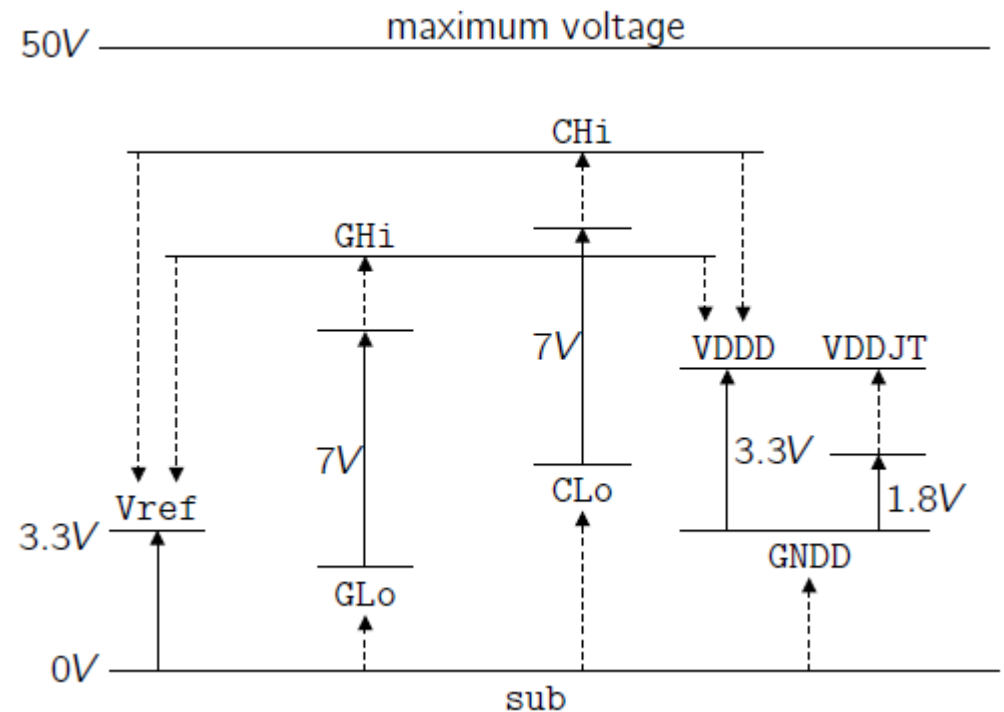
- floating supplies
 - sub has to be the lowest voltage
 - any voltage must not exceed 30V relative to sub (50V not yet tested)
 - Vref has to be sub+3.3V
 - VDDD and VDDJT relative to GNDD
 - VDDJT supports from 1.8V to 3.3V supply (1.8V tested)
- measured power consumption
 - VDDD@12.5MHz: 4mA
 - GNDD@12.5MHz: -8mA
 - VDDJT: 60 μ A
 - Vref: 170 μ A
 - sub: 12 μ A




- Slow Control
 - Configuration Register
 - Bias Current setting for sleep and boost states of level shifters
 - reserved bits for features not implemented in this chip revision
 - majority voter
 - triple redundancy in configuration bits
 - register can be read back to check for SEU
- Boundary Scan
 - read value of input pads and set output pads
 - allows to check connectivity of bumps
 - read and set I/Os from and to logic core
- All features have been tested ok @ 1.8V I/O voltage

- The strobe logic allows 2 modes for gate outputs:
 - non-overlapping gate
 - overlapping gate
- controlled by timing of strobe signal relative to falling clk edge
 - strobe can only switch gate on
 - gate is switched off automatically when gate of next row is switched on
- row skip
 - omit strobe signal while keeping clk running
 - last active row stays active
- clear strobe
 - gate has to be switched on
 - full control of clear output: switch-on and switch-off


non-overlapping gate

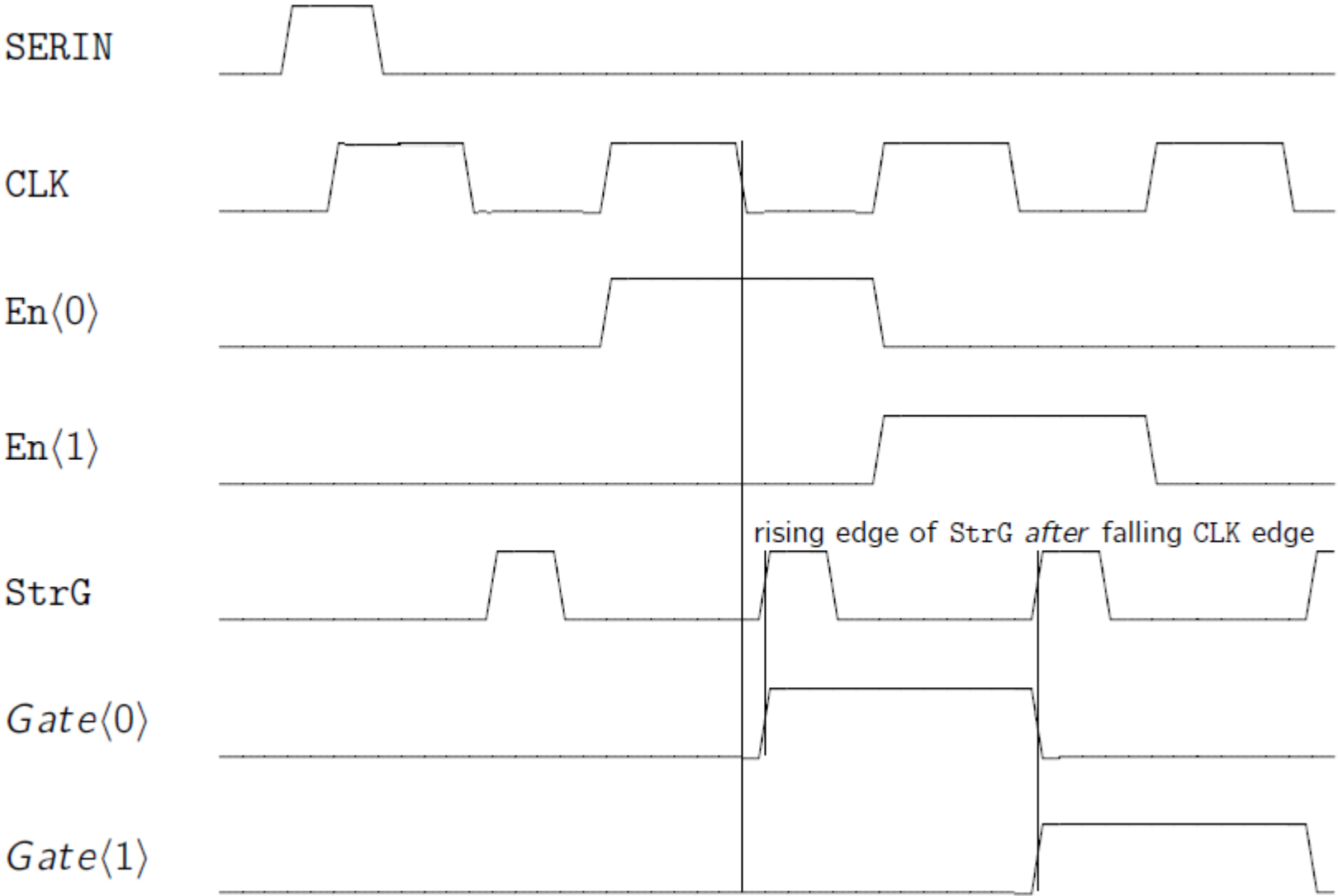

overlapping gate

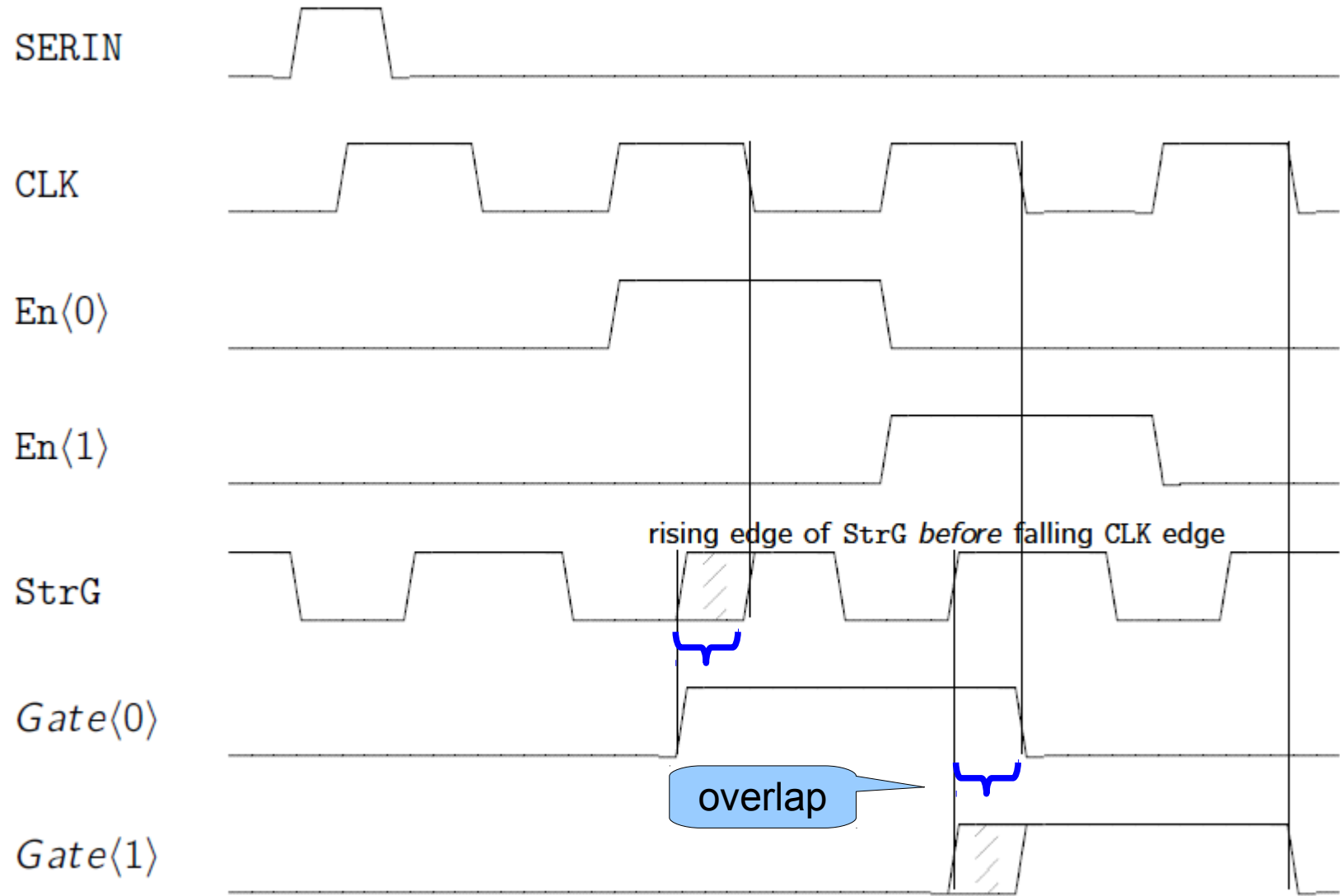


row skip

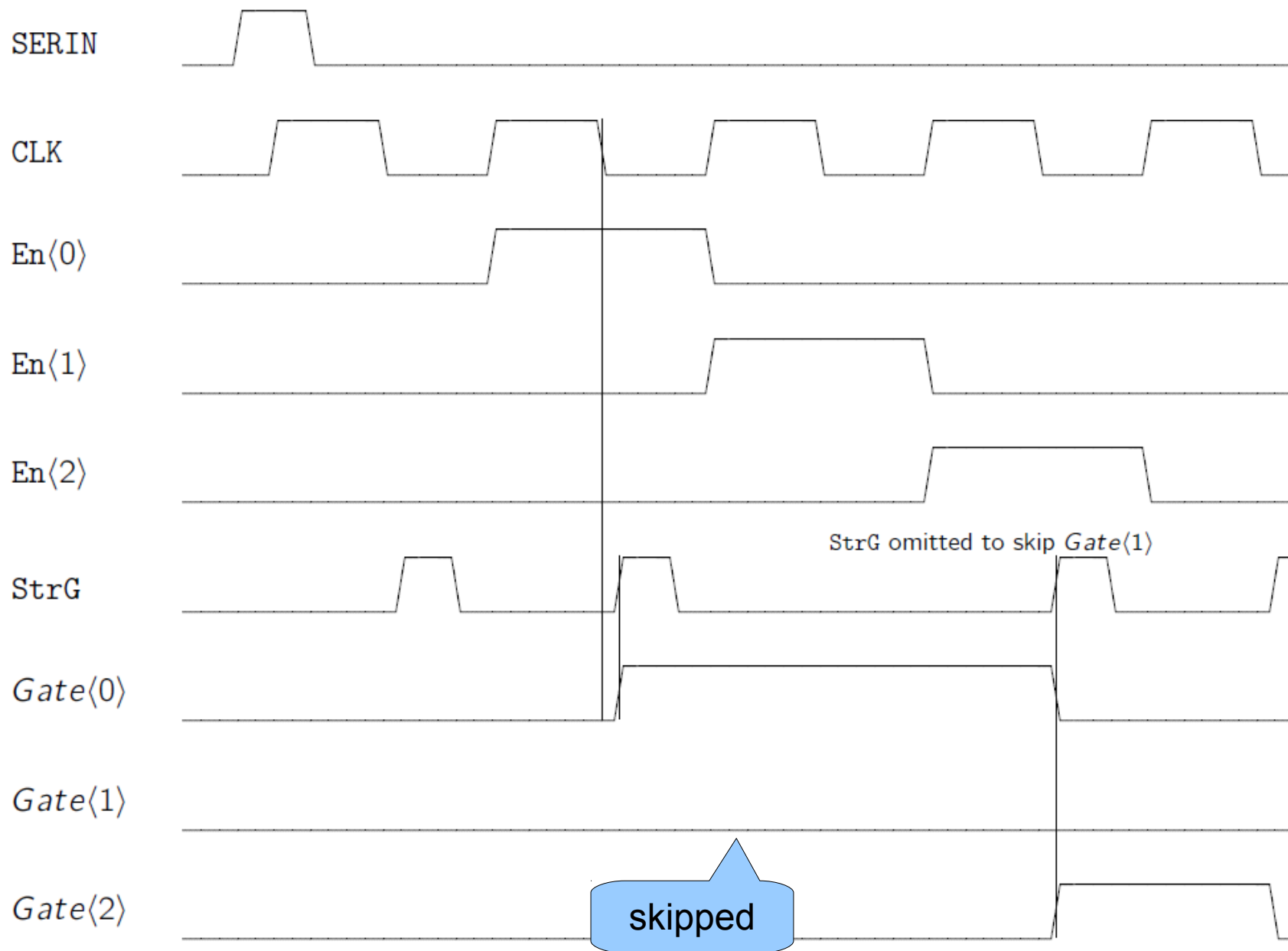


Test PCB

 - TestPCB for DCD-B and Switcher-B
- connects to FPGA board from Bonn
- Switcher-B wirebonding of I/O signals and some outputs (tricky!)
- load capacitors of 22pF, 47pF and 68pF



Measured current in digital supply

 


80ns




falling edge

 - 9V swing
- 10%-90%
 - 8pF: 1.9ns
 - 30pF: 5.3ns
 - 55pF: 7.9ns
 - 76pF: 9.8ns
 - 98pF: 12.1ns




rising edge

 
- 9V swing
- 10%-90%
 - 8pF: 1.9ns
 - 30pF: 5.1ns
 - 55pF: 7.8ns
 - 76pF: 9.8ns
 - 98pF: 12.6ns




80ns row time, 98pF load

 


overlapping gates

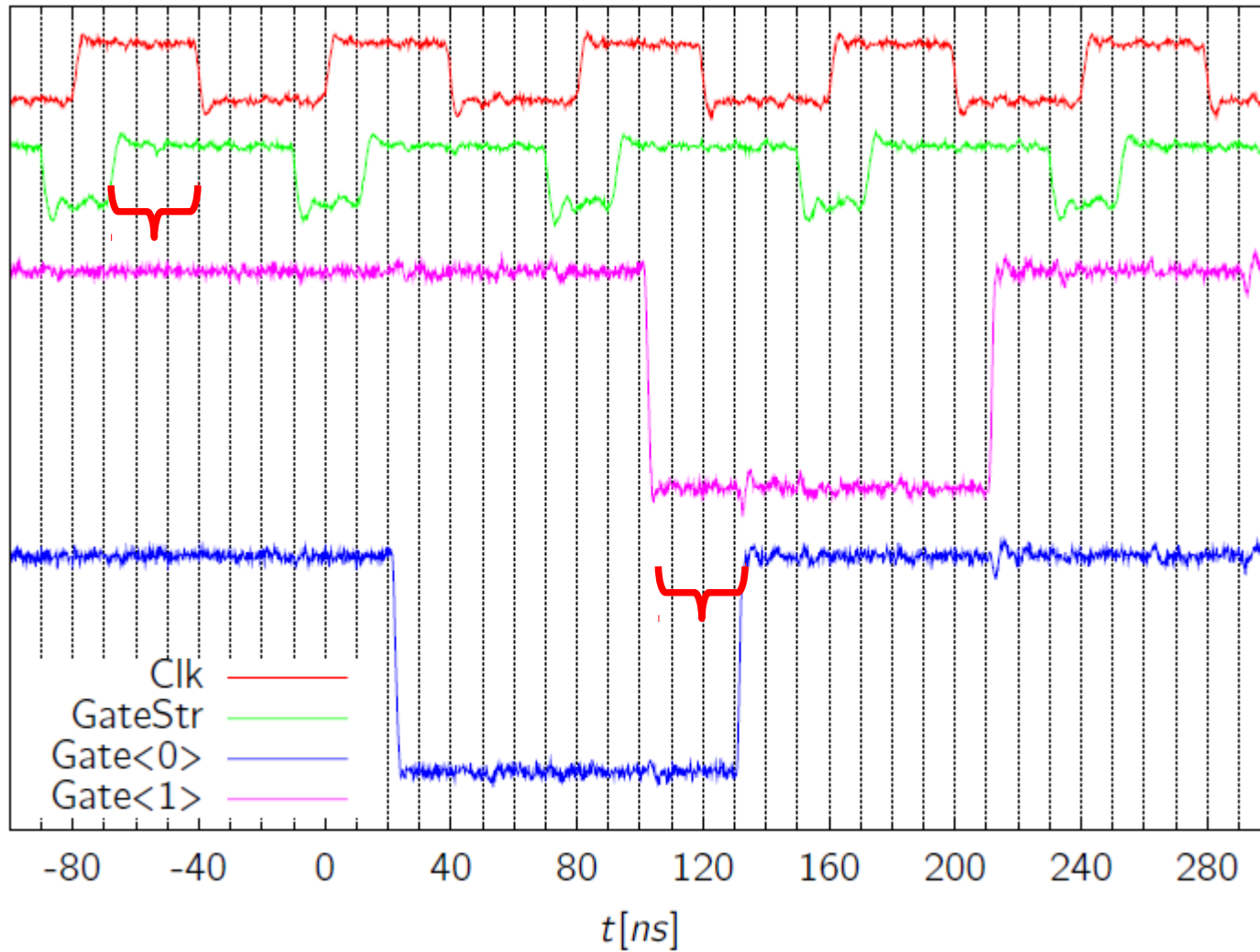


sample-clear-sample

 

sample-clear-sample 98pF

 

single sampling

 

Bias Settings


- set via JTAG
- delay between strobe signals and output
- influence on power consumption
- see manual for details

- Karlsruhe X-ray
 - 60kV; 33mA; Fe-filter; 115mm distance
 - 636krad/h
 - 24.5Mrad irradiated
- Switcher-B settings
 - 12.5MHz row frequency
 - VDDD=3.3V
 - VDDJTAG=1.8V
 - I_{bias}=6.6μA
 - I_{biasBoost}=210μA
 - GateHi=ClearHi=9V
 - Load Capacity=76pF

Gate Output

76pF
load!


Switcher-B Gate

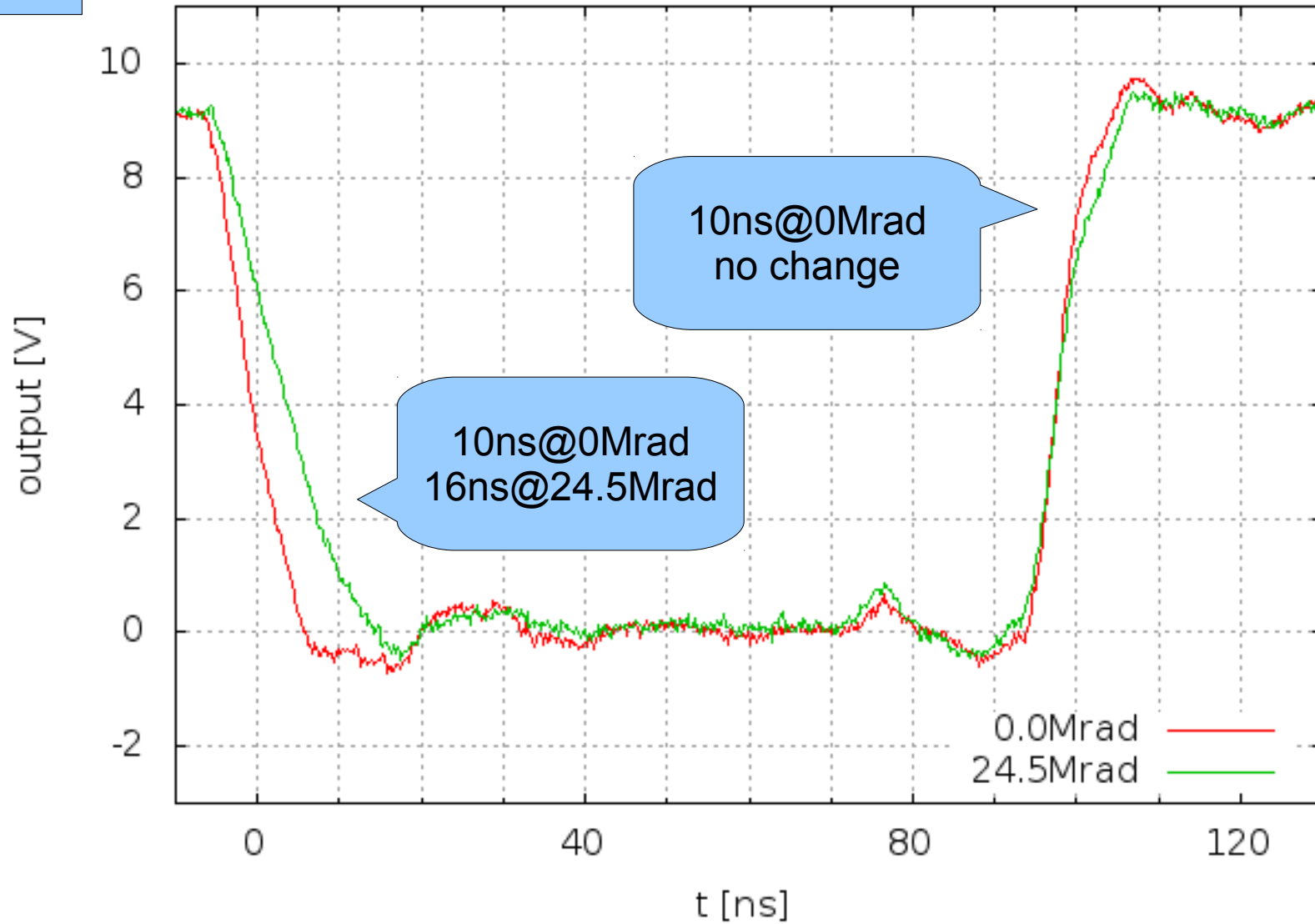

Clear Output

76pF
load!

Switcher-B Clear

 

10ns@0Mrad
5ns@24.5Mrad

10ns@0Mrad
12ns@24.5Mrad

0.0Mrad
24.5Mrad

- running at 12.5MHz (80ns)
- Irradiation:
 - within first 500krad
 - VDDD: **5mA** → 35mA
 - Vgate+Vclear: **13mA** → 26mA
 - within next 6Mrad back to normal
 - 24.5Mrad
 - VDDD: **4mA**
 - Vgate+Vclear: **11mA**

Conclusion

- Switcher-B working at 80ns row time
- JTAG slow control & boundary scan working
- Chip works after 24.5Mrad irradiation

- Next chip revision
 - add onchip termination resistors
 - adjustable current in LVDS
 - real LVDS output
 - decoupling capacitors to Vsource

- See Reference Manual for details
 - will be released next week

Thank you!